




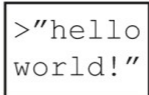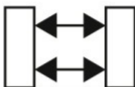
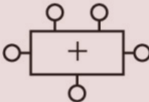

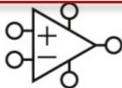


# COMP2300-COMP6300-ENGN2219

## Computer Organization & Program Execution

Convener: Shoaib Akram  
[shoaib.akram@anu.edu.au](mailto:shoaib.akram@anu.edu.au)



Australian  
National  
University

Application Software		Programs
Operating Systems		Device Drivers
Architecture		Instructions Registers
Micro-architecture		Datapaths Controllers
Logic		Adders Memories
Digital Circuits		AND Gates NOT Gates
Analog Circuits		Amplifiers Filters
Devices		Transistors Diodes
Physics		Electrons


**Broadening our horizon  
"one layer at a time"**

# We Covered Combinational Blocks

- Computation
  - Adders
  - ALU
  - Comparator
- Control
  - Multiplexer
  - Decoder
  - Tri-state Buffer
- Standard form (SOP)
- Boolean equation to 2-level implementation

 
# What will we learn this week?

- Circuits that can store information
  - State and clock
  - Cross-coupled inverter
  - SR latch
  - D latch
  - D flip-flop
  - Register & Memory
- Synchronous sequential circuits
  - Finite state machines
- Synchronous vs. Asynchronous sequential circuits



# Circuits that Store Information


# All Computers Need Memory to Work

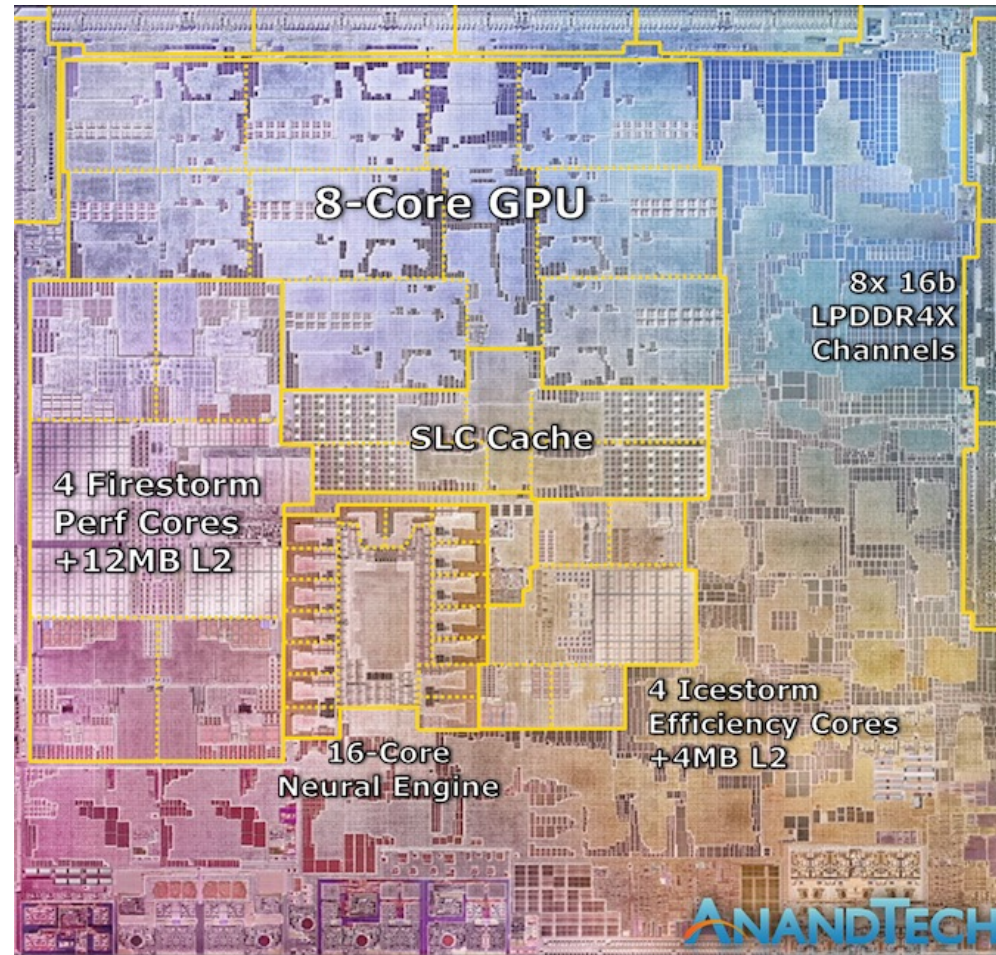

Apple M1,  
2021

Source: <https://www.anandtech.com/show/16252/mac-mini-apple-m1-tested>


# Large Portion of a System is Memory

 

[https://download.intel.com/newsroom/kits/40thanniversary/gallery/images/Pentium\\_4\\_6xx-die.jpg](https://download.intel.com/newsroom/kits/40thanniversary/gallery/images/Pentium_4_6xx-die.jpg)

Intel Pentium 4, 2000

# Large Portion of a System is Memory

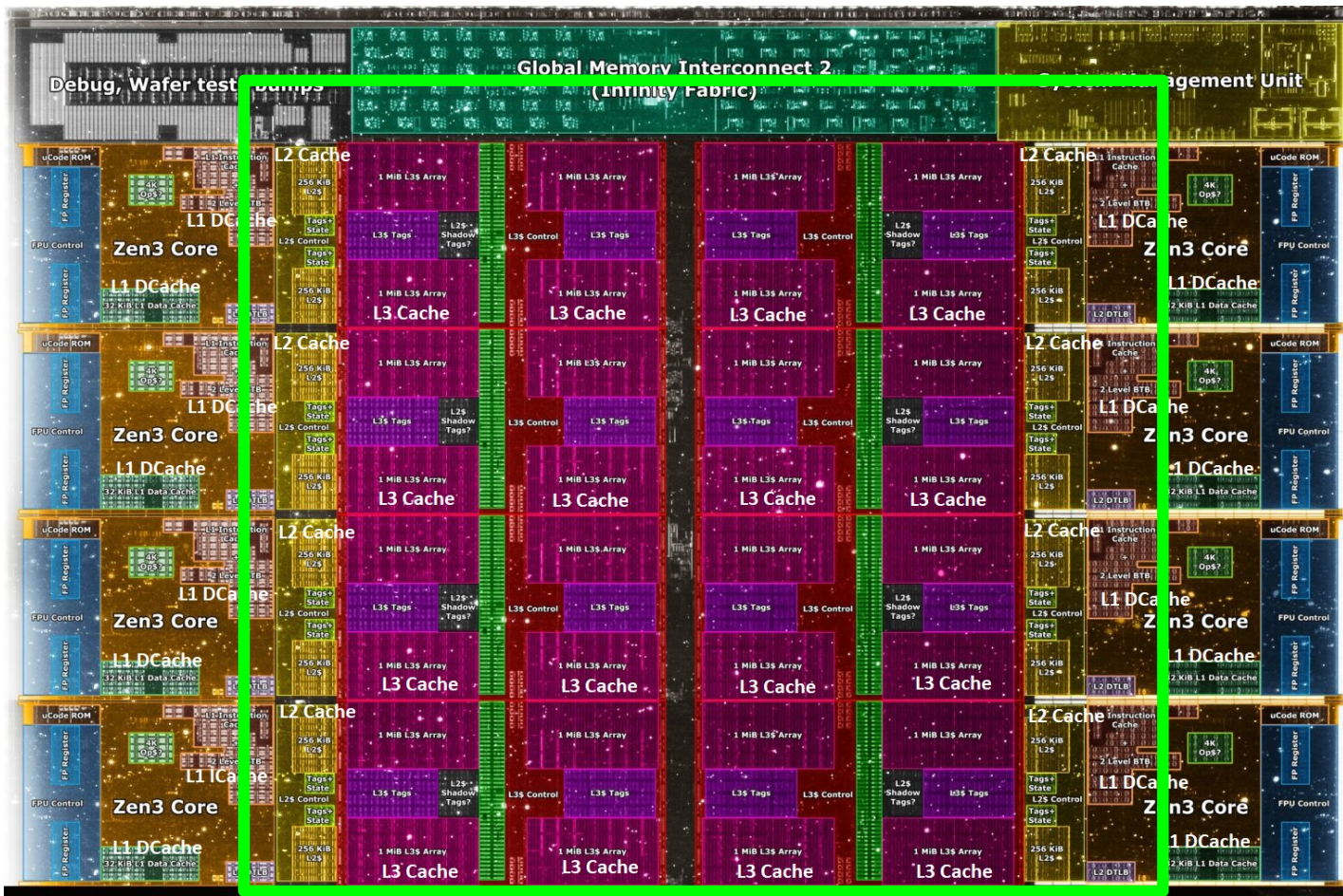

Core Count:  
8 cores/16 threads

L1 Caches:  
32 KB per core

L2 Caches:  
512 KB per core

L3 Cache:  
32 MB shared

AMD Ryzen 5000, 2020



# Large Portion of a System is Memory

IBM POWER10,  
2020

Cores:


15-16 cores,  
8 threads/core

L2 Caches:

2 MB per core

L3 Cache:


120 MB shared

 

<https://www.it-techblog.de/ibm-power10-prozessor-mehr-speicher-mehr-tempo-mehr-sicherheit/09/2020/>

# Large Portion of a System is Memory

Nvidia Ampere,  
2020

 

Cores:  
128 Streaming Multiprocessors


L1 Cache or Scratchpad:  
192KB per SM  
Can be used as L1 Cache and/or  
Scratchpad

L2 Cache:  
40 MB shared

# Motivation

- **Combinational** circuit output depends **only** on **current** input **combinations**
- We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- **How can we design a circuit that stores information?**

# Sequential Circuit

 

The output depends on the input combinations and the state of the system

# What is State?

- What is **state**?
  - A **set of bits** that **summarize** past behavior of system
  - The **set of bits** are called **state variables**
  - Each bit is stored in a state or memory element
- The state of a system ***informs us everything about the past we need to know to predict the future***
- The output of sequential logic depends on both the current input values and the **state** of the system

# Example of State

- Consider a **controller** for a traffic light



- To set the **next** state, the controller needs to remember the **current** state
- The past input values (signals from traffic sensors) are summarized by the “**current**” state stored as a **2-bit** value

# Another Example

- We remember the meaning of the **words** in time **t** since
  - we remembered them in time **t - 1**
    - all the way back to the point of time
      - when we first committed them to **memory**

# Capturing State

- To **remember** or to store the **state** of the system (current state of traffic light), we need a **logic element** with memory
  
- **How can we capture input data and persist it until the next input?**





# Capturing and Storing One Bit

- **One bit of information represents two possible states**
- To store one bit, we need
  - An element with two stable states (**bistable** element)
  - The ability to change the state
- First, we will find the bistable element
  - And then focus on the *ability to change state*
  
# Bistable element


- The fundamental building block of **memory** is a **bistable element** with two stable states



Cross-coupled inverters: A pair of inverters connected in a loop

# Analysis of Bistable Element


- **How should we analyze circuits with cyclic paths?**
  - When the circuit is switched on,  $Q$  is either **0** or **1** (**scenarios**)
  - **Show:** Output is stable (**consequence – A**)
  - **Show:**  $Q$  and  $Q'$  are complements of each other (**consequence – B**)
- **Scenario # 1:  $Q = 0$  (FALSE)**
  - $I_2$  receives **0**,  $Q' = 1$ : **B** is satisfied
  - $Q' = 1$ ,  $Q = 0$ , **A** is satisfied
  - Consistent with original assumption
- **Scenario # 2:  $Q = 1$  (TRUE)**
  - $I_2$  receives **1**,  $Q' = 0$ : **B** is satisfied
  - $Q' = 0$ ,  $Q = 1$ , **A** is satisfied

 

Section 3.2 of H&H

 
# Bistable Element: Observations

- **Bistable element has two stable states**
  - Stores one bit of information
- **Q** reveals about past, necessary to explain the future
  - If **Q = 0**, it will remain **0** forever
  - If **Q = 1**, it will remain **1** forever
- The (**initial**) state of the bistable element is unpredictable when **powered on**
  - Bistable element is *not practical* because the user lacks inputs to control its state
  - **We need something else!**


 
# SR Latch

- Two **cross-coupled NOR** gates
- The **state** can be **controlled** with S/R inputs
  - **S** = Set to **1**
  - **R** = Reset to **0**



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


- NOR gate revision
  - When both inputs are **0**, the output is **1**
  - If any of the inputs is **1**, the output is **0**

# SR Latch: Analysis

- SR latch has inputs *unlike the cross-coupled inverter*
- Four scenarios in the truth table (Sim = Simultaneous)

Scenario	S	R	Q	Q'
Sim-0	0	0		
Reset	0	1		
Set	1	0		
Sim-1	1	1		

# Whiteboard: SR Latch

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

S	R	Q
0	0	
0	1	
1	0	
1	1	

Section 3.2.1 of H&H

# SR Latch: Analysis

- **Scenario # 1 (Reset):**  $R = 1, S = 0$ 
  - N1 sees at least one **TRUE (1)** input
    - $Q = \text{FALSE (0)}$
  - N2 sees both Q and S **FALSE**
    - $Q' = \text{TRUE (1)}$
- **Scenario # 2 (Set):**  $R = 0, S = 1$ 
  - N1 sees **0** and  $Q'$ 
    - What is  $Q'$ ?
  - N2 sees at least one **TRUE** input
    - $Q' = \text{FALSE (0)}$
  - Revisit N1 ( $R = 0$  and  $Q' = 0$ )
    - $Q = \text{TRUE (1)}$





# SR Latch: Analysis

- **Scenario # 3 (Sim-1): R = 1, S = 1**
  - N1 sees at least one TRUE (1) input
    - Q = FALSE (0)
  - N2 sees at least one TRUE (1) input
    - Q' = FALSE (0)
  
- **Scenario # 4 (Sim-0): R = 0, S = 0**
  - N1 sees 0 and Q'
    - What is Q'?
  - N2 sees 0 and Q
    - What is Q?
  - **We are stuck!**
    - Wait: remember the cross-coupled inverter? Q can be 0 or 1 😊
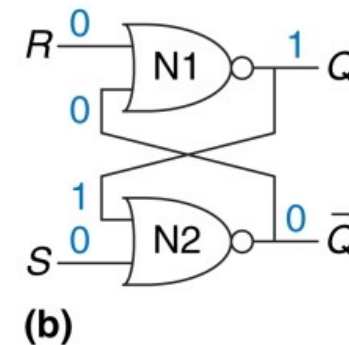 
# SR Latch: Analysis

- Scenario # 4-A (Sim-0):  $R = 0, S = 0, Q = 0$ 
  - N2 sees  $S = 0$  and  $Q = 0$ 
    - $Q' = 1$
  - N1 sees one TRUE (1) input
    - $Q = 0$  (hindsight:  $Q$  is indeed 0 as assumed)
- Scenario # 4-B (Sim-0):  $R = 0, S = 0, Q = 1$ 
  - N2 sees  $Q = 1$ 
    - $Q' = \text{FALSE}$
  - N1 receives two FALSE inputs
    - $Q = 1$  (hindsight:  $Q$  is indeed 1 as assumed)



# SR Latch: Analysis Summary


- SR latch has inputs **unlike the cross-coupled inverters**
- Four scenarios in the truth table (**Sim** = Simultaneous)

Scenario	S	R	Q	Q'
Sim-0	0	0	Q <sub>prev</sub>	Q' <sub>prev</sub>
Reset	0	1	0	1
Set	1	0	1	0
Sim-1	1	1	0	0

# SR Latch: Observations

- SR latch is a **bistable element** but its state can be controlled
  - To **set** a bit means to make it **TRUE**
  - To **reset** is to make it **FALSE**
- **Q** accounts for the entire history of past inputs
  - All *prior set/reset patterns* are irrelevant
  - The *most recent set/reset* event predicts the future behavior of the **SR** latch
- Asserting both **set/reset** to **1** does not make sense
  - Neither intuitively nor physically
  - The circuit outputs **0** on **Q** and **Q'** which is inconsistent
  - **We need something else!**

SR Latch  
Symbol

 

**Next: D Latch**


First, We Will Learn to Model the  
Progression of Time

# Representing Time

- Physicist and philosopher's view
  - Relentless arrow continuously progressing forward
  - Changes in the world can be infinitesimally small

*Arrow of time*  
*Changes continuously*

 
- **Too mysterious and deep for computer scientists**
  - We prefer a **discrete** representation
  - Break time into **fixed-length** intervals called **cycles**
  - cycle 1, cycle 2, cycle 3, and so on .... **Cycles are indivisible and atomic**



Changes in the world occur only during cycle transitions; within cycles, the world stands still
 
# Time in Digital Systems

- Periodic **square wave (clock)** generated by a special circuit
- Used to *synchronize* state updates everywhere in the system



$$\text{Frequency} = 1/T_c$$

**Changes in the world** occur only during cycle transitions. Within cycles, the world stands still

# Time in Digital Systems

- Our goal is to endow logic circuits with the ability to
  - **Maintain state over time**
  - **Respond to time changes**




# D Latch

- **Two drawbacks of SR latch**
  - Strange behavior when **S = 1** and **R = 1**
  - **S** and **R** inputs serve two roles: *what* the state is and *when* the state changes
- Designing sequential circuits is **easier** when we have control over *when* the state changes
- The **D latch** **overcomes** the two drawbacks
  - A data input (**D**) *controls what* the next state should be
  - The clock input (**CLK**) controls *when* the state should change

Section 3.2.2 of H&H

# D Latch

 


- **Scenario # 1:**  $CLK = 0, S = 0, R = 0, D = X$ 
  - The value of **D** is irrelevant
  - $Q = Q_{prev}$  (remember the old value)

Latch is opaque (blocks new data from flowing to Q)
- **Scenario # 2:**  $CLK = 1, D = 0, S = 0, R = 1$ 
  - The latch is **reset**

Latch is transparent (acts like a buffer)
- **Scenario # 3:**  $CLK = 1, D = 1, S = 1, R = 0$ 
  - The latch is **set**


# Whiteboard: D Latch

 

S	R	Q
0	0	$Q_{\text{prev}}$
0	1	0
1	0	1
1	1	0

Section 3.2.2 of H&H

# D Latch: Truth Table

 


Scenario	CLK	D	Q	Q'
Opaque	0	X	$Q_{\text{prev}}$	$Q'_{\text{prev}}$
Transparent/0	1	0	0	1
Transparent/1	1	1	1	0

Section 3.2.2 of H&H

# D Latch: Observations

- D latch is a **level-triggered** or a **level-sensitive** circuit
  - Reacts to the level (0 or 1) of the CLK input
- D latch avoids the **awkward** case of both **S/R** asserted
- D latch **changes** its state **continuously** when **CLK = 1**
- Designing **correct & efficient** sequential circuits is easier when
  - the state changes only at a **specific instant** in time instead of **changing continuously**
  - **We need something else!**

D Latch  
Symbol

 

# Summary

- **Cross-coupled inverter**
  - Two stable states *but* no **inputs** to control the state
- **SR Latch**
  - Two control inputs: **S** for **Set** (**1**) and **R** for **Reset** (**0**)
  - Awkward when **S** = **1** and **R** = **1**
  - The state changes instantly (*need greater control over when it changes*)
- **D Latch**
  - One **D**ata input (**D**) and one control input (**CLK**)
  - Level-sensitive: **CLK** = **1** (**Transparent**), **CLK** = **0** (**Opaque**)
  - Output (**Q**) changes continuously when **CLK** = **1**

# D Flip-Flop


- **Problem with D Latch:** The output changes *continuously* when **CLK = 1**
  - This behavior leads to timing bugs and circuits that are difficult to analyze
- **D flip-flop** is an **edge-triggered** circuit
  - Sets its **state** to the **data input** when **CLK** changes from **0** to **1**
  - At all other times, the D flip-flop remembers its **state**

Flip-flop samples the input at the edge of the clock



 
# Analogy: Photography

- Input: **D**, Output/State: **Q**
- **CLK** = Clock (periodic square wave)




 
*Sample the input just at the rising edge (copy D to Q)*




  
# D Flip-Flop


- Two back-to-back D latches controlled by complementary clocks
- The L1 latch is the master and L2 is the slave latch
  - Remember that, when **CLK = 0**, D latch is *opaque*
  - And, when **CLK = 1**, D latch is *transparent*



D Latch
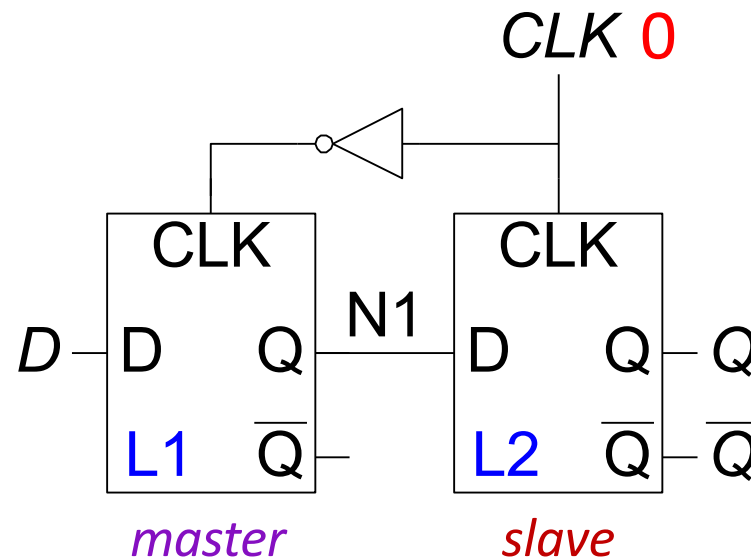
# D Flip-Flop: Analysis


- **CLK = 0**
  - master: transparent
  - slave: opaque



***The value at D propagates through to N1, but Q is cut off from N1***
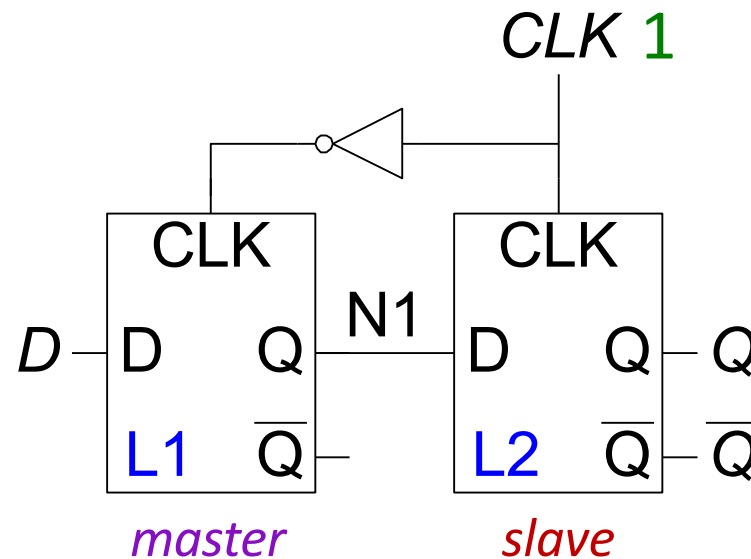
# D Flip-Flop: Analysis

- **CLK = 1**
  - master: opaque
  - slave: transparent



*The value at N1 propagates through to Q, but N1 is cut off from D*

# D Flip-Flop: Observations


- The value at **D** immediately before the **CLK** rises from **0** to **1** get copied to **Q** immediately after **CLK** rises
- At all other times, **Q** retains its **old** value
  - There is an *opaque* latch blocking **D** from flowing to **Q**

A **D** flip-flop copies **D** to **Q** on the *rising/falling edge* of the **CLK**, and remembers its state at all other times

# Other Names


- All names means the same
  - Master-slave flip-flop
  - Edge-triggered flip-flop
  - Positive edge-triggered flip-flop

## D Flip-Flop Symbols

 


# Remember the Symbols

D Latch  
Symbol

 


D Flip-Flop  
Symbols

 

# Register
 
# Register


- How can we use flipflops to store more than one bit?
  - Principle of **modularity**: Use more flipflops!
  - A single **CLK** to simultaneously write to all flipflops



- **Register**: A structure that stores more than **one bit** of information and can be **read from** and **written to**
- This **register** holds **4 bits**, and its data is referenced as **Q[3:0]**





# 4-bit Register

 

To build an **N-bit** register, use a bank of **N** flipflops with a shared **CLK**

# 4-bit Register

  

**This line represents 4 wires**

**This register stores 4 bits**

# Register Width


- Register width is the number of flipflops in a register
  - Typical register widths: 8-bit, 16-bit, 32-bit, 64-bit, ..., 512+ bits today
  - Register width is an important parameter of any computer
- **Why do we need wide registers with large widths?**
  - Solving **large/important** problems require manipulating large numbers
  - Large numbers need large number of bits, hence more flipflops
  - Floating point numbers (**section 5.3**) with decimal point require extra bits
- **Question:** Do we need 512-bit registers in microwave controller, automobile engine control unit (ECU), computer used in financial tech, cockpit domain controller in cars?

**Now, We will See**


**Different Types of Flipflops**
 
# Enabled Flip-Flops

- Loads a new value on a specific clock edge
- Inputs: **CLK**, **D**, **EN**
  - The enable input (**EN**) controls when new data (**D**) is stored
- **Function:**
  - **EN** = **1**: D passes through to Q on clock edge
  - **EN** = **0**: the flip-flop retains its previous state





Symbol

 

  
# Clock Gating

- Doing an **AND** of **CLK** with **EN** is called **clock gating**
- **Caution:** Performing logic on clock is best avoided
  - AND gate delays the clock
  - If **EN** changes while **CLK** is **1**, the flipflop sees a **glitch** (switch at an incorrect time)



 
# Resettable Flip-Flop

- Add another input (**RESET**)
- **Function:**
  - **RESET** = 1 (ignore **D** and reset output to 0)
  - **RESET** = 0 (ordinary D flip-flop)



- **Two types**

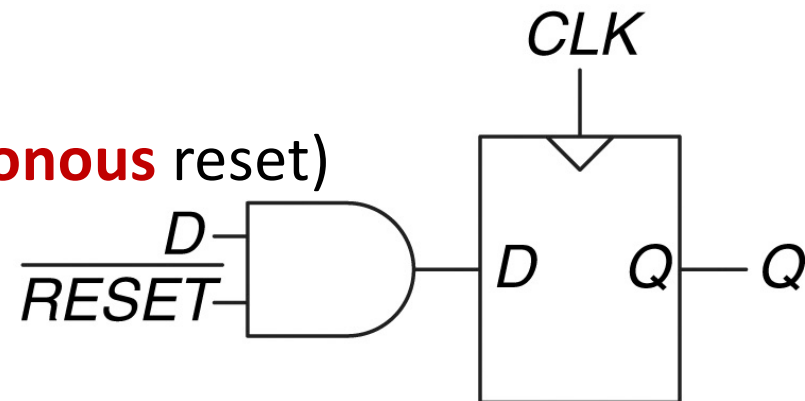- Reset on clock edge only (**synchronous** reset)





- Reset immediately (**asynchronous** reset) **Homework exercise!**

# Settable Flip-Flop

- Add another input (**SET**)
- **Function:**
  - **SET** = 1 (**Q** is set to 1)
  - **SET** = 0 (ordinary D flip-flop)

## Symbols

  




**Examples:**

Latch vs. Flipflop

# Example - I

 

Q (Latch)

Q (Flipflop)

T0

T0

T1

T1


T2

T2

T3

T3

# Example - I

 

Q (Latch)

T0 0 FALSE

T1

T2

T3

Q (Flipflop)


T0 0 FALSE

T1

T2

T3

# Example - I

 

Q (Latch)

T0 0 FALSE

T1 1 TRUE

T2

T3

Q (Flipflop)


T0 0 FALSE

T1 1 TRUE

T2

T3

# Example - I

 

**Q (Latch)**

**T0** 0 FALSE

**T1** 1 TRUE

**T2** 1 TRUE

**T3**

**Q (Flipflop)**


**T0** 0 FALSE

**T1** 1 TRUE

**T2** 1 TRUE


**T3**

# Example - I

 

	Q (Latch)	Q (Flipflop)
T0	0 FALSE	T0 0 FALSE
T1	1 TRUE	T1 1 TRUE
T2	1 TRUE	T2 1 TRUE
T3	0 FALSE	T3 1 TRUE

# Example - II

 

Q (Latch)

T0

T1

T2

T3

Q (Flipflop)


T0

T1

T2

T3

# Example - II

 

Q (Latch)

T0 1 TRUE

T1

T2

T3

Q (Flipflop)

T0 0 FALSE


T1

T2

T3




# Example - II

 

	<u>Q (Latch)</u>
T0	1 TRUE
T1	0 FALSE
T2	
T3	

	<u>Q (Flipflop)</u>
T0	0 FALSE
T1	1 TRUE
T2	
T3	


# Example - II

 

	<u>Q (Latch)</u>
T0	1 TRUE
T1	0 FALSE
T2	1 TRUE
T3	

	<u>Q (Flipflop)</u>
T0	0 FALSE
T1	1 TRUE
T2	1 TRUE
T3	

# Example - II

 

	<u>Q (Latch)</u>
<b>T0</b>	1 TRUE
<b>T1</b>	0 FALSE
<b>T2</b>	1 TRUE
<b>T3</b>	1 TRUE

	<u>Q (Flipflop)</u>
<b>T0</b>	0 FALSE
<b>T1</b>	1 TRUE
<b>T2</b>	1 TRUE
<b>T3</b>	0 FALSE

# Memory

# Memory

- Houses have **unique addresses**
  - In computers, everything is binary **0** or **1** so **addresses** are in binary as well
- Houses have stuff inside them
  - In computers, the **“only”** type of stuff is binary data
  - Binary data can be program variables, photos, videos, emails, word documents



# Memory

A huge number of **uniquely identifiable** *locations* each **storing** a piece of **information**

# Memory

**Address:** Naming or identification scheme

**VS.**

**Data:** Information stored inside a location

# Memory

How many **locations**?

How big is the **piece of information** at each location?

Which **technology** is used to store information?



# Memory

- **Memory** is made up of locations that can be written to or read from. An example memory array with 4 locations:

<b>Addr(00):</b>	0100 1001	<b>Addr(01):</b>	0100 1011
<b>Addr(10):</b>	0010 0010	<b>Addr(11):</b>	1100 1001


- Each unique memory location is indexed with a unique **address**. 4 locations require 2 address bits ( $\log[\text{\#locations}]$ )
- **Addressability**: the number of **bits** of information stored **in each location**. This example: addressability is 8 bits
- The entire set of **unique locations** in memory is referred to as the **address space**

# Memory

- **Memory** in almost all computers today is *byte addressable* due to historical reasons (later)
- Typical memory is **MUCH** larger consisting of billions of locations
- Two billion locations and **8-bit (1 byte)** addressability
  - Address space is **2 GB** or **2 billion 1-byte** locations
- Uniquely identifying each byte of memory *allows individual bytes of stored information* to be changed easily
 
# Addressing Memory


- **Let's implement a simple memory array with:**
  - 3-bit addressability & address space of 2 (total of 6 bits)
- **How can we select an address to read?**
  - Two addresses so address size is  $\log(2) = 1$  bit



## 6-Bit Memory Array

<b>Addr(0)</b>	<b>Bit<sub>2</sub></b>	<b>Bit<sub>1</sub></b>	<b>Bit<sub>0</sub></b>
<b>Addr(1)</b>	<b>Bit<sub>2</sub></b>	<b>Bit<sub>1</sub></b>	<b>Bit<sub>0</sub></b>


# Reading from Memory

 


- Each “box” is a **bit cell** storing one bit
  - Can be enabled (like the enabled flip-flop with **EN**)
  - Takes an **input** ( $D_i$ ) and produces an output (**D**)

# Reading from Memory


Addr[0]

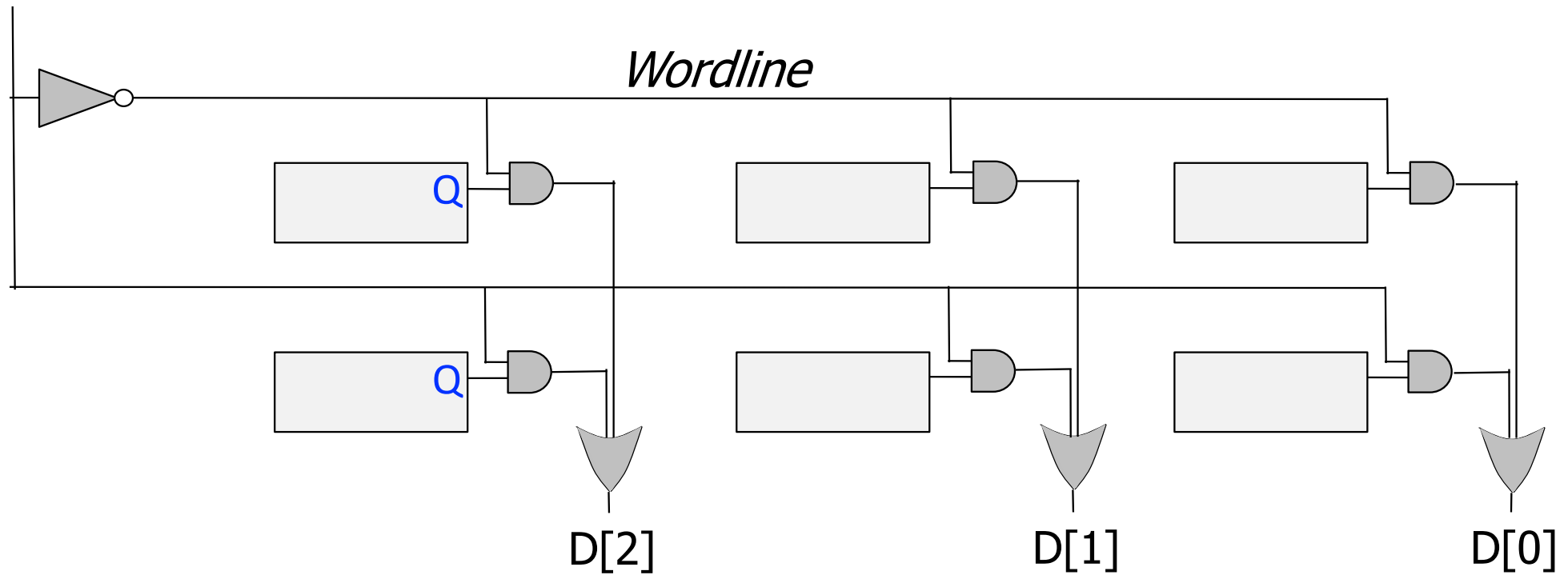


# Reading from Memory

 

# Reading from Memory

 


# Reading from Memory

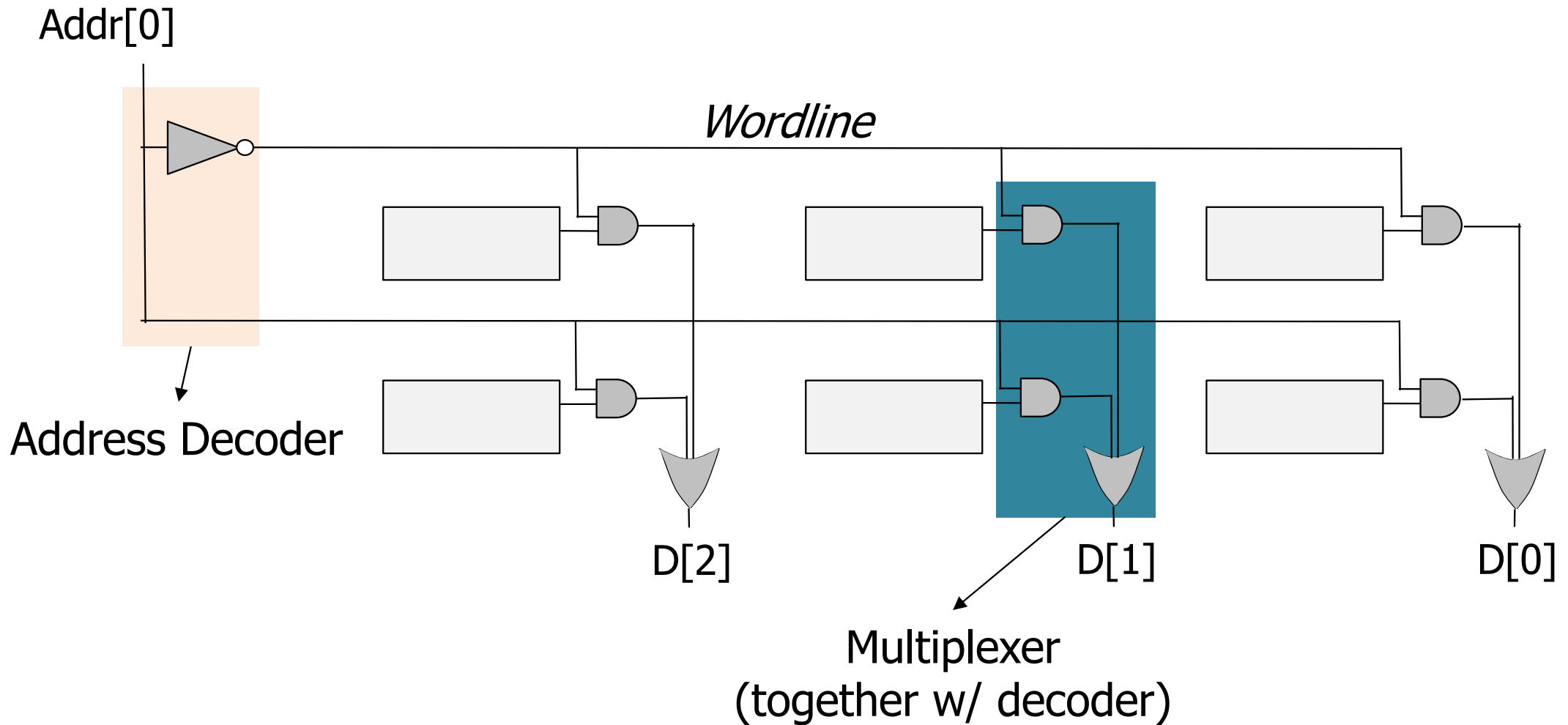




# Reading from Memory

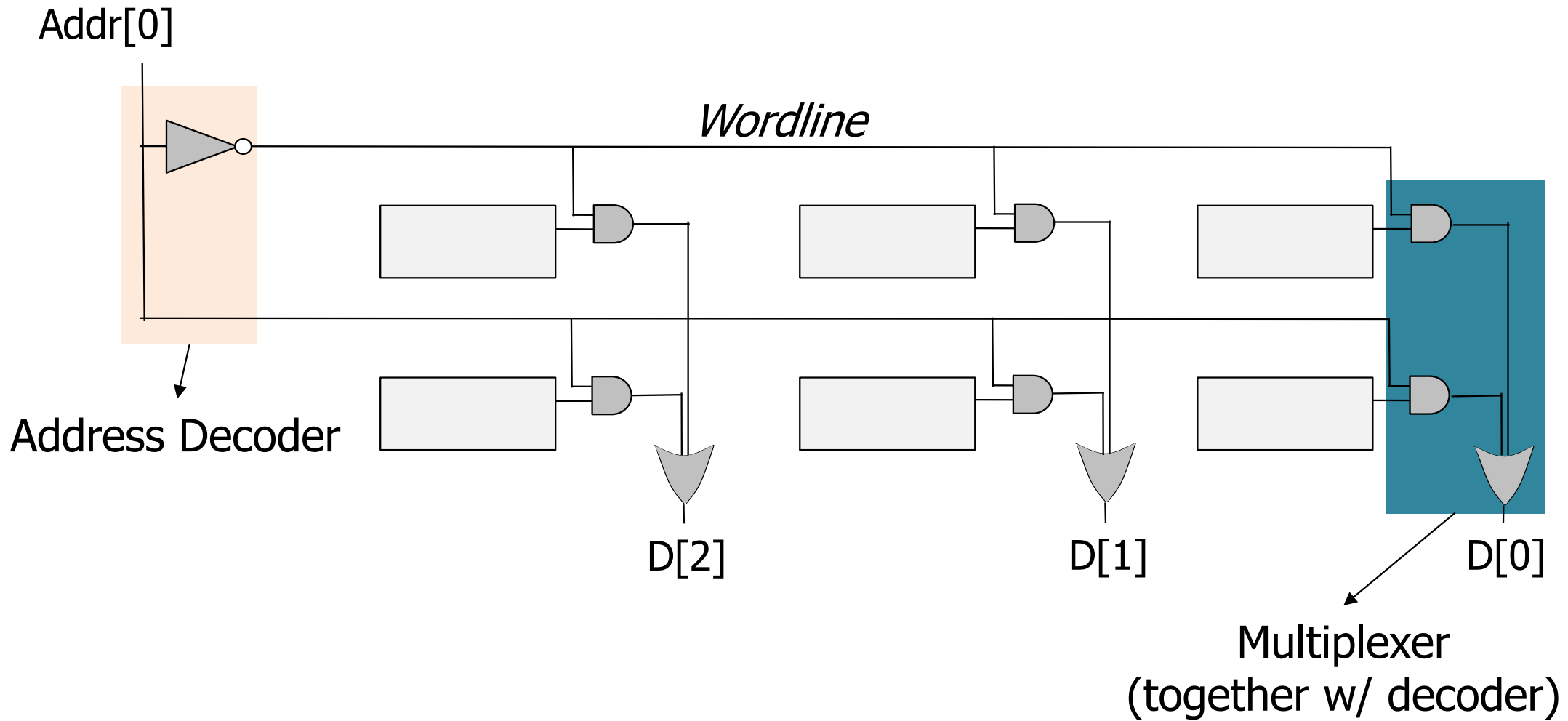

# Recall: Multiplexer (MUX), or Selector


- **Selects** one of the  $N$  inputs to connect it to the output
  - based on the value of  $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX

$$Y = D_0 \bar{S} + D_1 S$$

 

 
# Writing to Memory

- **How can we select an address to write to it?**
  - How should we tell memory our intention to write?
    - We assert the **EN** input of the enabled flip-flop
  - How should we tell memory what data we need to write?
    - We use the **D<sub>i</sub>** input of the flip-flop



 
# Writing to Memory

- How can we select an address to write to it?
  - Input is indicated with  $D_i$



 
# Writing to Memory

- How can we select an address to write to it?
  - Input is indicated with  $D_i$



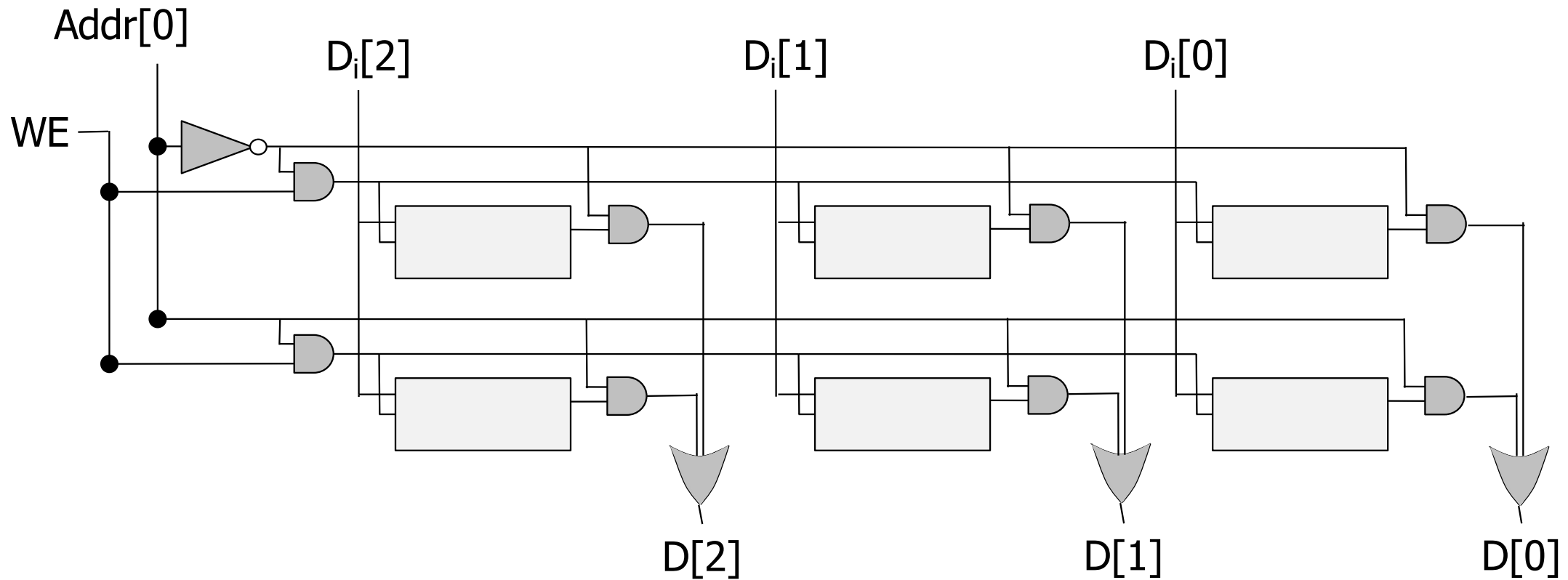
# Full Memory Array

- Both reading from and writing to a memory array




# A Bigger Memory Array

4 locations X 3 bits

 



 

# Example: Reading Location 3


 




Figure 3.21 Reading location 3 in our 2<sup>2</sup>-by-3-bit memory.
 
# Recall: Decoder

- The decoder is useful in determining how to interpret a bit pattern
  - It could be the address of a location in memory, that the processor intends to read from
  - It could be an instruction in the program and the processor needs to decide what action to take (based on *instruction opcode*)




# Recall: A 4-to-1 Multiplexer

 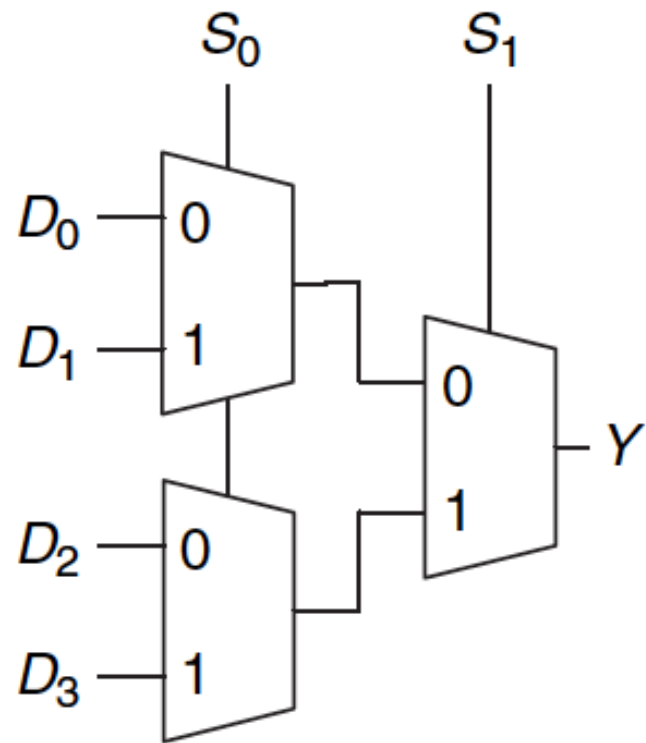

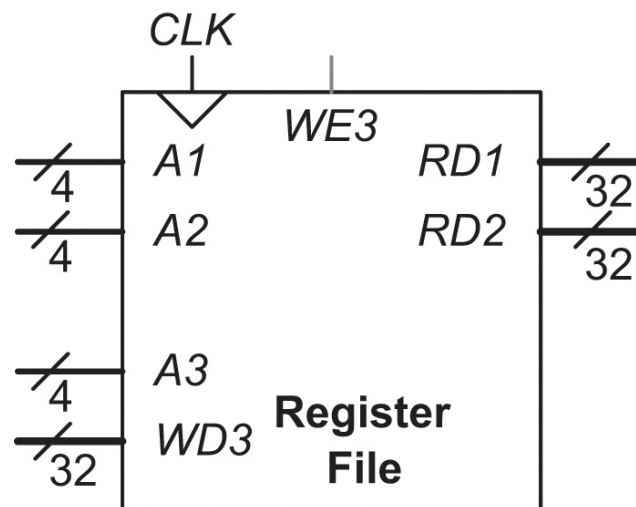
# Multi-Ported Memory

- Each port gives read/write access to one memory address
- Typically, we need to access many addresses simultaneously
  - Example with two **read** ports and one **write** port


 
# Another Representation of Memory

- What is the memory's **addressability**?
- How big is the **address space**?



# Sequential Logic Circuits

- **Week 1 & 2:** Combinational circuits that process information
- **Week 3:** Boolean algebra, & circuits that can store information, & basic storage elements, & memory
- **Now,** digital logic structures that can **both** process information (i.e., make decisions) **and** store information
  - **The decision is based on both input combinations and their history**

# Sequential Logic Circuits

- We have discovered circuit elements that can **store information**
- Now, we will use these elements to build circuits that **remember past inputs**



## Combinational

Only depends on current inputs

[https://www.easykeys.com/228\\_ESP\\_Combination\\_Lock.aspx](https://www.easykeys.com/228_ESP_Combination_Lock.aspx)  
<https://www.fosmon.com/product/tsa-approved-lock-4-dial-combo>



## Sequential

Opens depending on past inputs




# State

- In order for this lock to work, it has to **remember** past events
- If passcode is **R13-L22-R3**, *sequence of states* to unlock
  - A. Locked and no operations have been performed
  - B. Locked but **R13** completed
  - C. Locked but **R13 – L22** completed
  - D. Unlocked and **R13 – L22 – R3** completed
- The **state** of a system is a snapshot of all relevant elements of the system at the moment of the snapshot
  - To open the lock, **states A–D must be completed in order**
  - If anything else happens (L5 or L6), lock **returns** to state A


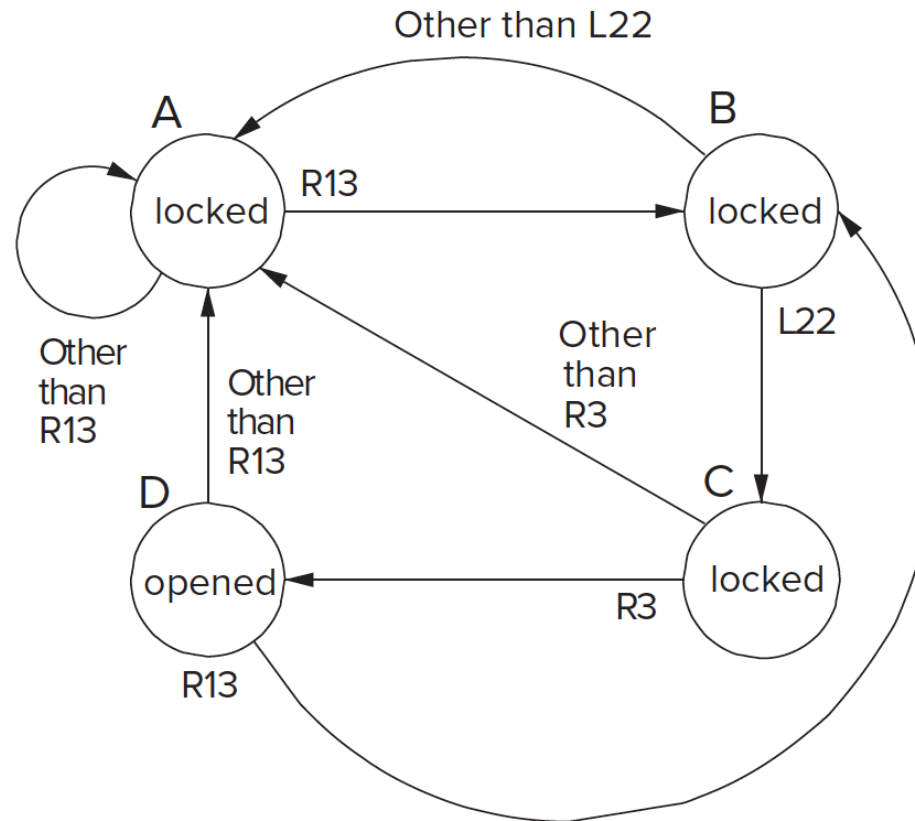
# State Diagram of Sequential Lock

- Completely describes the operation of the sequential lock



# Another Example: Soft Drink Machine

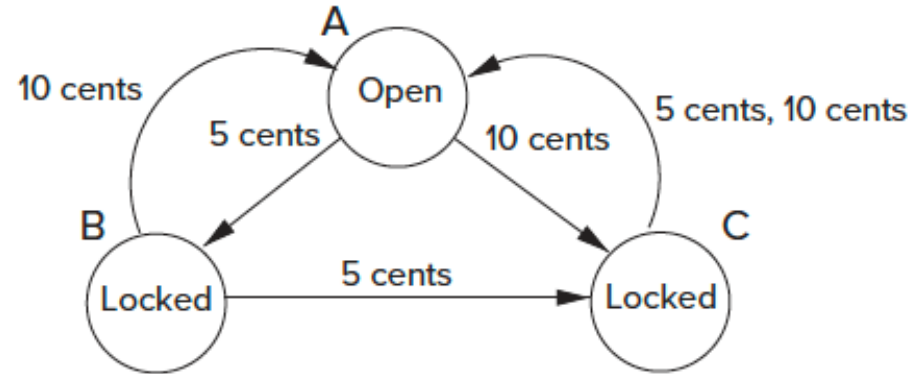


Figure 3.27 State diagram of the soft drink machine.

- There are only **three** possible states
  - A. The lock is open, so a bottle can be (or has been) removed
  - B. The lock is not open, but 5 cents have been inserted.
  - C. The lock is not open, but 10 cents have been inserted.

# Another Example: Soft Drink Machine

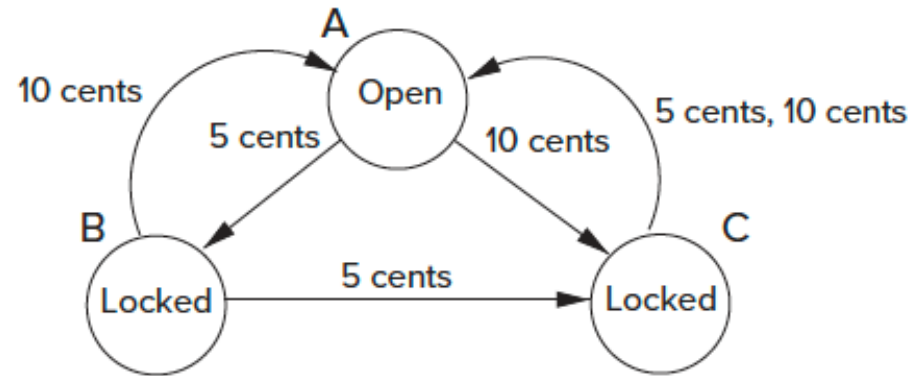


Figure 3.27 State diagram of the soft drink machine.

- One possible sequence of states is as follows

 




Image source: Patt and Patel, "Introduction to Computing Systems", 2<sup>nd</sup> ed., page 84.

# Another Example: Traffic Light

- There are only three possible states:

- A. Green
- B. Yellow
- C. Red


- The sequence of states is as follows

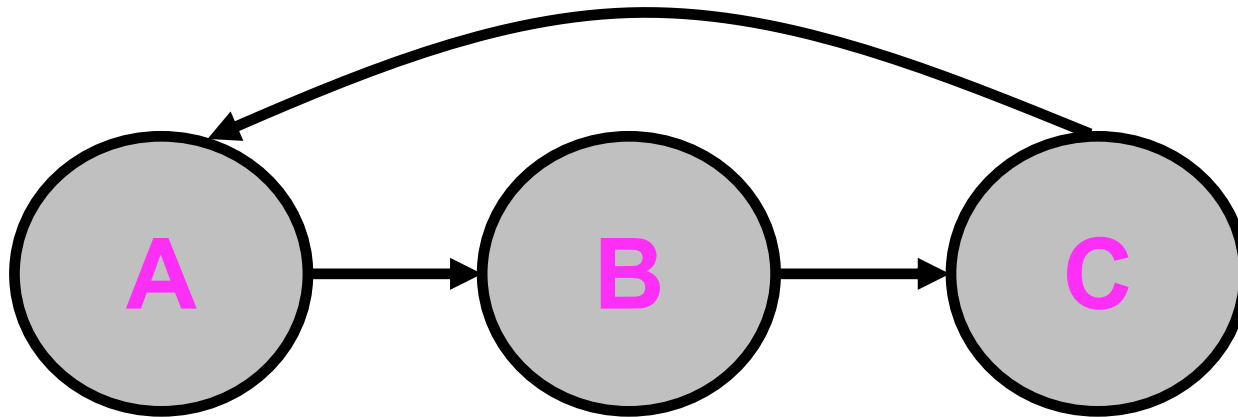 

# Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an **asynchronous** machine
  - State transition occur when they occur
  - There is nothing that *synchronizes* when each state transition must occur
- Most modern computers are **synchronous** machines
  - State transitions take place after fixed units of time
  - Controlled by the clock that dictates when transitions occur
- These are two different design paradigms, with **tradeoffs**

# Changing State & The Notion of Clock

 


- When should the vending machine change state from **A** to **B**?
- When should the traffic light change from one state to another?

# Changing State & The Notion of Clock

- When should the machine change state from **A** to **B**?
- We need a **clock** to dictate when to change state
  - Clock alternates between **0** & **1**



- At the start of a clock cycle (  ), system state changes
  - During a clock cycle, the **state stays constant**
  - The machine stays in a specific state an **equal amount of time**



# Changing State & The Notion of Clock

- **Clock** is a general mechanism that **triggers transition from one state to another** in a (**synchronous**) sequential circuit
- Clock **synchronizes state changes** across many sequential circuit elements
- Combinational logic evaluates for the length of the clock cycle
- Clock cycle should be chosen to accommodate maximum combinational delay

# Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an **asynchronous** machine
  - State transition occur when they occur
  - There is nothing that synchronizes when each state transition must occur
- Most modern computers are **synchronous** machines
  - State transitions take place after fixed units of time
  - Controlled in part by a clock, as we will see soon
- These are two different design paradigms, with **tradeoffs**
  - Synchronous control can be easier to get correct when the system consists of **many components and many states**
  - Asynchronous control can be more efficient (no clock **overheads**)

**We will assume synchronous systems in this course**

"the art of directing the **simultaneous** performance of several players or singers by the use of gesture." Wikipedia, Conducting



**We will assume synchronous systems in this course**

# Why are Arbitrary Sequential Circuits a Bad Idea?


Reading: Section 3.4 of H&H

# Arbitrary Sequential Circuits

- **Important:** We need to **discipline** ourselves and only build synchronous sequential circuits
- State is **synchronized** at the clock edges
- Let's examine two arbitrary sequential circuits
 
# Ring Oscillator

- What does the circuit below do?
  - One output, No inputs**




- X **oscillates** b/w **0** and **1** (prove it assuming  $X = 0$ )
  - No stable state (**Unstable** or **Astable**)
- If the propagation delay of each inverter is **1 ns**, then the clock period is 6 ns

Example 3.3 of H&H

# Asynchronous D Latch

- What does the circuit below do?
  - CLK = D = 1 (*transparent*, Q = 1)
  - CLK = 0 (Q = Q<sub>prev</sub>)

$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$

 


Example 3.4 (page 119) of H&H

# Asynchronous D Latch

- What does the circuit below do?
  - CLK = D = 1 (*transparent*, Q = 1)
  - CLK = 0 (Q = Q<sub>prev</sub>)

CLK	D	Q <sub>prev</sub>	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$

 


Example 3.4 (page 119) of H&H



# Asynchronous D Latch

- What if  $t_{INV} \gg t_{AND}$  and  $t_{INV} \gg t_{OR}$ ?
  - Node N1 and Q may both fall before  $\overline{CLK}$  changes
    - Q gets **stuck** at 0
  - **Race condition:** The path through **CLK to Q** is **faster** than  $\overline{CLK}$  to Q

 


Example 3.4 (page 119) of H&H

# Takeaways

- When outputs are fed back directly back to inputs, these are called **cyclic** paths
- Combinational logic has **NO** cyclic paths
  - Outputs settle after **propagation** delay
- Circuits with cyclic paths are called **asynchronous** circuits
  - **Difficult to analyze**
  - **Timing issues (race conditions, oscillations)**
  - **May work in one set of conditions but not in another**

# Synchronous Sequential Circuits


- What is the problem with asynchronous circuits?
  - *Cyclic paths lead to races and unstable behavior*
- **Solution:** Break the cyclic paths by **inserting** registers somewhere in the path
- Registers contain **state**, and **synchronized** to the clock

 

Section 3.3.2 of H&H
 
# Synchronous Sequential Circuits


**General Rule:** *If the clock is sufficiently slow, so that the inputs to all registers settle before the next clock edge, all races are eliminated*



# Composition Rules

- Every circuit element is either a register or a combinational element
- At least one element is a register
- All registers receive the same clock signal
- Every cyclic path contains at least one register

# Which circuits are synchronous sequential?

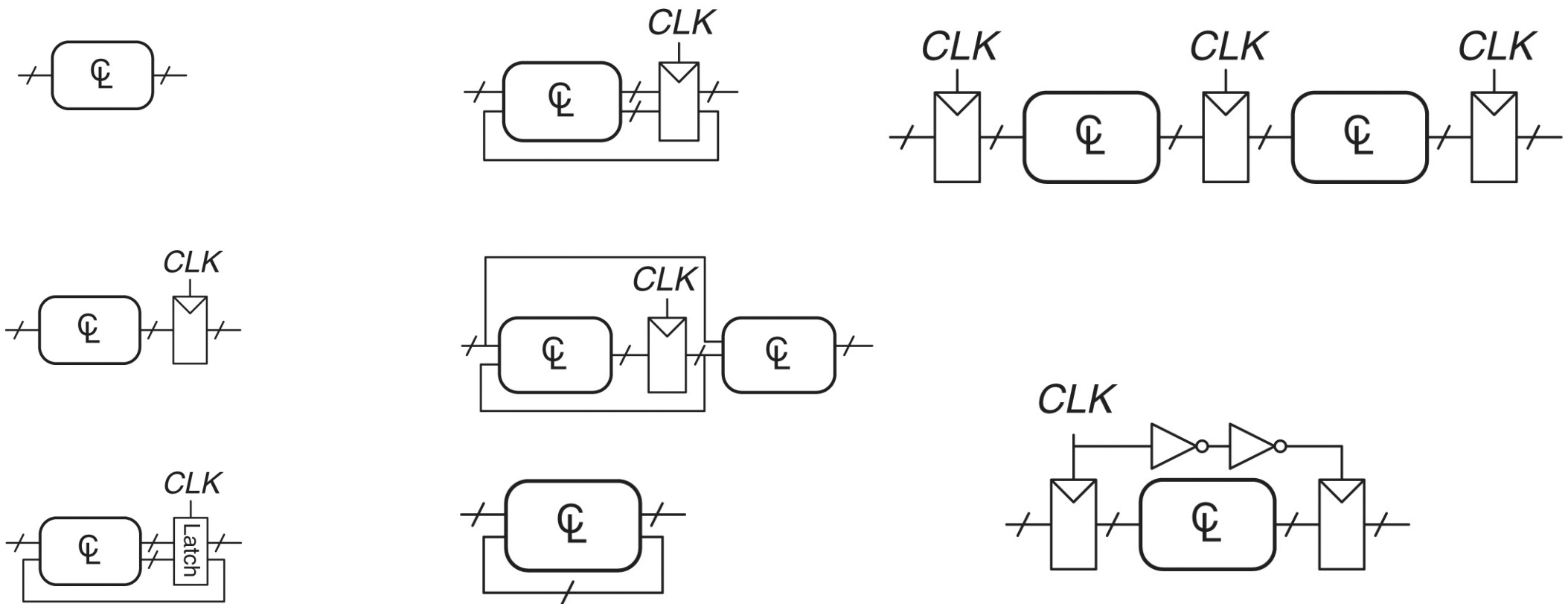

Example 3.5 of H&H

# Finite State Machines

---

**Compulsory** Reading: Section 3.4 of H&H

# Finite State Machines

- What is a **Finite State Machine** (FSM)?
  - **A discrete-time model** of a stateful system
  - A finite set of states a system can be in
- An **FSM** pictorially shows
  - The set of all possible states that a system can be in
  - How the system transitions from one state to another
- An **FSM** can model
  - A traffic light, an elevator, microwave, microprocessor, fan speed, car lock




# FSMs Consist of:

## ■ Five elements:

- A **finite** number of **states**
  - **State**: snapshot of all relevant elements of the system at the time of the snapshot
- A **finite** number of external **inputs**
- A **finite** number of external **outputs**
- An explicit **specification of all state transitions**
  - **How to get from one state to another**
- An explicit **specification of what determines each external output value**
  - If state is A, then output is 10
 
# Finite State Machines (FSMs)

- Each FSM consists of three separate parts:
  - next state logic
  - state register
  - output logic




# FSMs Consist of:

- **Sequential circuits**

- **State register(s)**

 
- Store the current state and
    - Provide the next state at the clock edge



- **Combinational Circuits**


- **Next state logic**

- Determines what the next state will be

 


- **Output logic**

- Generates the outputs

 

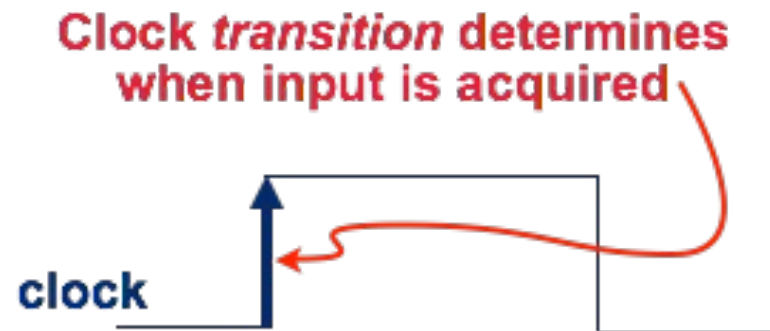
# State Register

- Why do we need flip-flops (**NOT latches**) to implement a **state register**
- Properties of state register
  - We need to store data at the **beginning** of every clock cycle



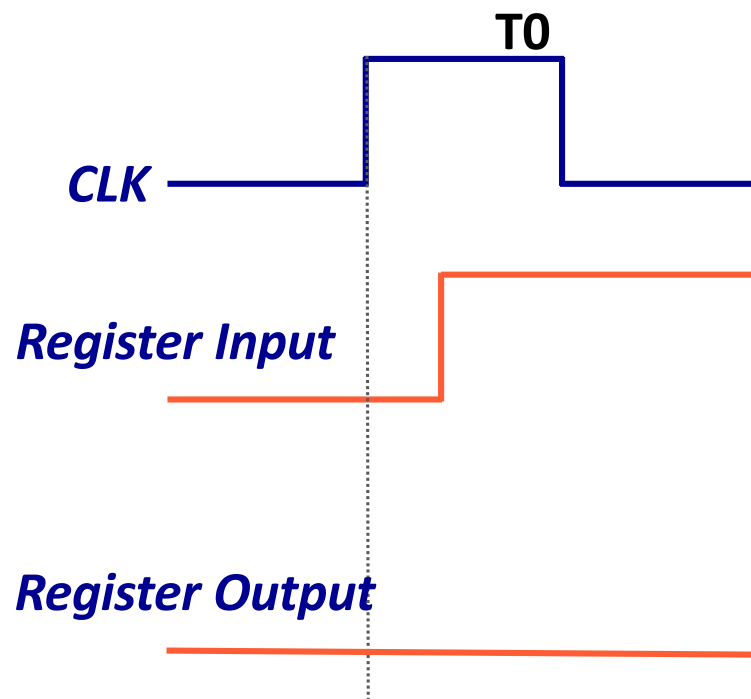
# State Register

- The data must be **available** during the **entire clock cycle**



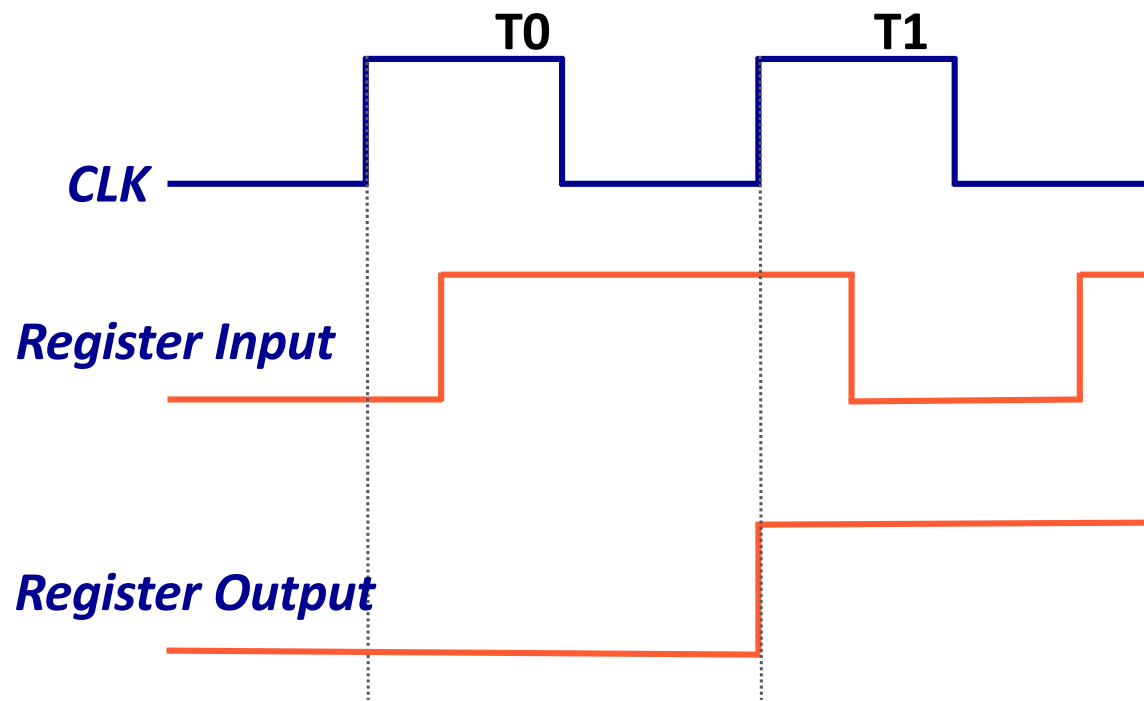
# State Register

- The data must be **available** during the **entire clock cycle**



 
# State Register

- The data must be **available** during the **entire clock cycle**


 
# State Register



- The data must be **available** during the **entire clock cycle**
  - So combinational elements have enough time to process input combinations




  
# The Problem with Latches

- We cannot simply wire a clock to **CLK** input of a latch
  - Whenever the clock is **HIGH**, the latch propagates **D** to **Q**
  - **The latch is transparent**



# State Register uses Flip-Flops

- D (input) is **observable** at Q (output) **only** at the **beginning of the next** clock cycle
- Q is **available for the full clock cycle**

# Implementing FSMs

## Traffic Light Controller

---

The Next Example is from H & H: Section 3.4

Acknowledgement: *Selection of Slides from Digital Design and Computer Architecture, Onur Mutlu, ETH Zurich, Spring 2022*


<https://safari.ethz.ch/digitaltechnik/spring2022/doku.php?id=schedule>

# Finite State Machines (FSMs)


- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state
  - **Mealy FSM**: outputs depend on the current state and inputs

# Moore & Mealy FSM

Moore FSM

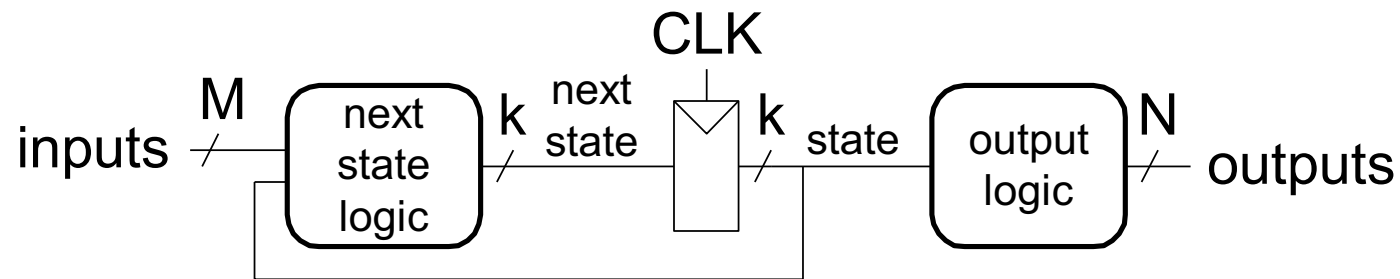


Mealy FSM

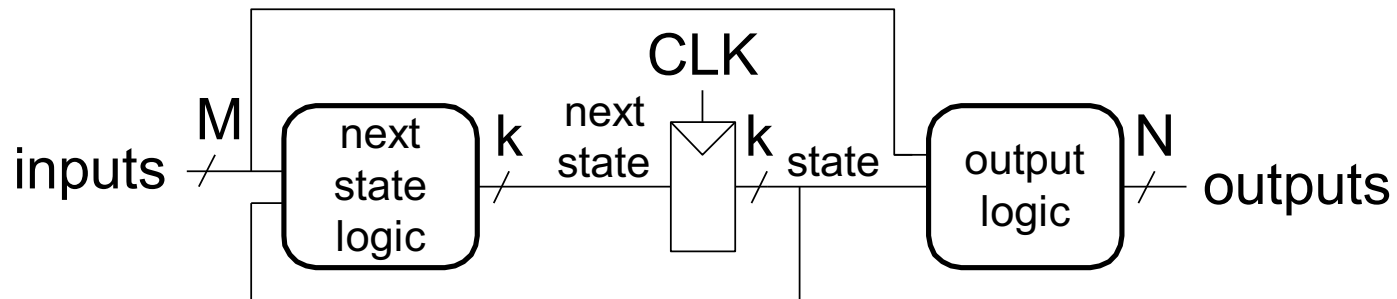
 
# Finite State Machine Example


- “Smart” traffic light controller
  - **2 inputs:**
    - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there’s traffic)
  - **2 outputs:**
    - Lights:  $L_A$ ,  $L_B$  (Red, Yellow, Green)
- State can change every 5 seconds
  - Except if **green** and traffic, stay **green**



From H&H Section 3.4.1
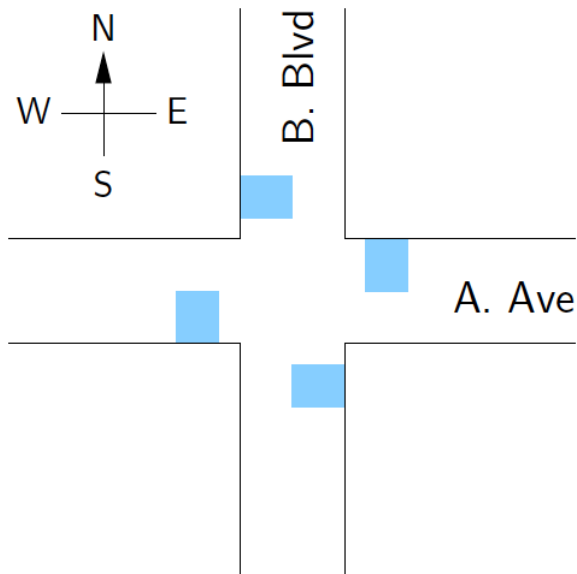
# Finite State Machine Example

- Traffic sensors are built into the road
- Each sensor indicates if a street is empty or there are vehicles nearby




$T_A = (\text{eastbound traffic on A}) \text{ OR } (\text{westbound traffic on A})$

$T_B = (\text{northbound traffic on B}) \text{ OR } (\text{southbound traffic on B})$
 
# Finite State Machine Example

- **Inputs  $T_A$  and  $T_B$** 
  - Returns **TRUE** if there are cars on the road
  - Returns **FALSE** if the road is empty
- **Outputs  $L_{A1:0}$  and  $L_{B1:0}$** 
  - Each set of lights receive 2-bit digital inputs from the traffic light controller specifying whether it should be: **RED**, **YELLOW**, **GREEN**




Output	Encoding
<b>GREEN</b>	00
<b>YELLOW</b>	01
<b>RED</b>	10



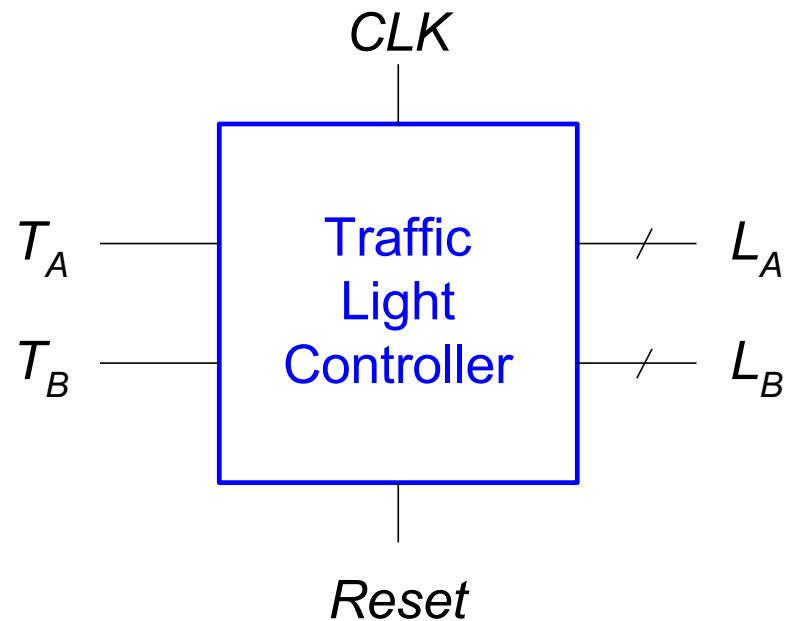
# Finite State Machine Blackbox

- **Inputs:** CLK, Reset,  $T_A$ ,  $T_B$
- **Outputs:**  $L_A$ ,  $L_B$


 
# Finite State Machine Diagram



- Moore FSM: outputs labeled in each state
  - States: Circles
  - Transitions: Arrows (Arcs)


  
# Finite State Machine Diagram



- Moore FSM: outputs labeled in each state
  - States: Circles
  - Transitions: Arrows (Arcs)

→ From “current state” **S0** to “next state” **S1**



 
 
# Finite State Machine Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arrows (Arcs)



 
 
# Finite State Machine Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arrows (Arcs)


  
# Finite State Machine Diagram


- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arrows (Arcs)



# Finite State Machine:

## State Transition Table


# FSM State Transition Table

 

Current State	Inputs		Next State
	$T_A$	$T_B$	
S	$T_A$	$T_B$	$S'$
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	




# FSM State Transition Table

 

Current State	Inputs		Next State
	$T_A$	$T_B$	
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0


# FSM State Transition Table

 

Current State	Inputs		Next State
S	T <sub>A</sub>	T <sub>B</sub>	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	00
S1	01
S2	10
S3	11


# FSM State Transition Table

 

Current State		Inputs		Next State	
S <sub>1</sub>	S <sub>0</sub>	T <sub>A</sub>	T <sub>B</sub>	S' <sub>1</sub>	S' <sub>0</sub>
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

# FSM State Transition Table

 


Current State		Inputs		Next State	
S <sub>1</sub>	S <sub>0</sub>	T <sub>A</sub>	T <sub>B</sub>	S' <sub>1</sub>	S' <sub>0</sub>
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

S'<sub>1</sub> = ?

# FSM State Transition Table

 


Current State		Inputs		Next State	
S <sub>1</sub>	S <sub>0</sub>	T <sub>A</sub>	T <sub>B</sub>	S' <sub>1</sub>	S' <sub>0</sub>
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\bar{S}_1 \cdot S_0) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B) + (S_1 \cdot \bar{S}_0 \cdot T_B)$$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = ?$$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

# FSM State Transition Table

 

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \text{ xor } S_0 \quad \text{(Simplified)}$$


$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$



# Finite State Machine:


## Output Table

# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow


# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 


$$L_{A1} = S_1$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 


$$L_{A1} = \overline{S_1}$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 

$$L_{A1} = \overline{S_1}$$


$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 

$$L_{A1} = \overline{S_1}$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1 \cdot S_0$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1


Output	Encoding
green	00
yellow	01
red	10

# Finite State Machine:


## Schematic




# FSM Overview

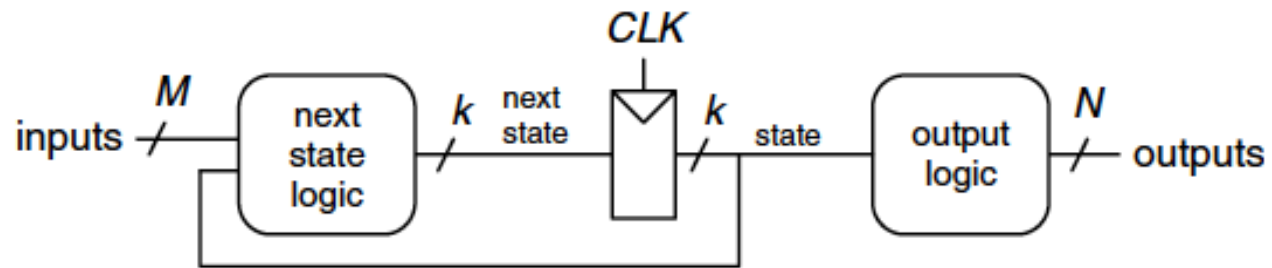

# FSM Schematic: State Register

 


# FSM Schematic: Next State Logic

 

$$S'_1 = S_1 \text{ xor } S_0$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

# FSM Schematic: Output Logic

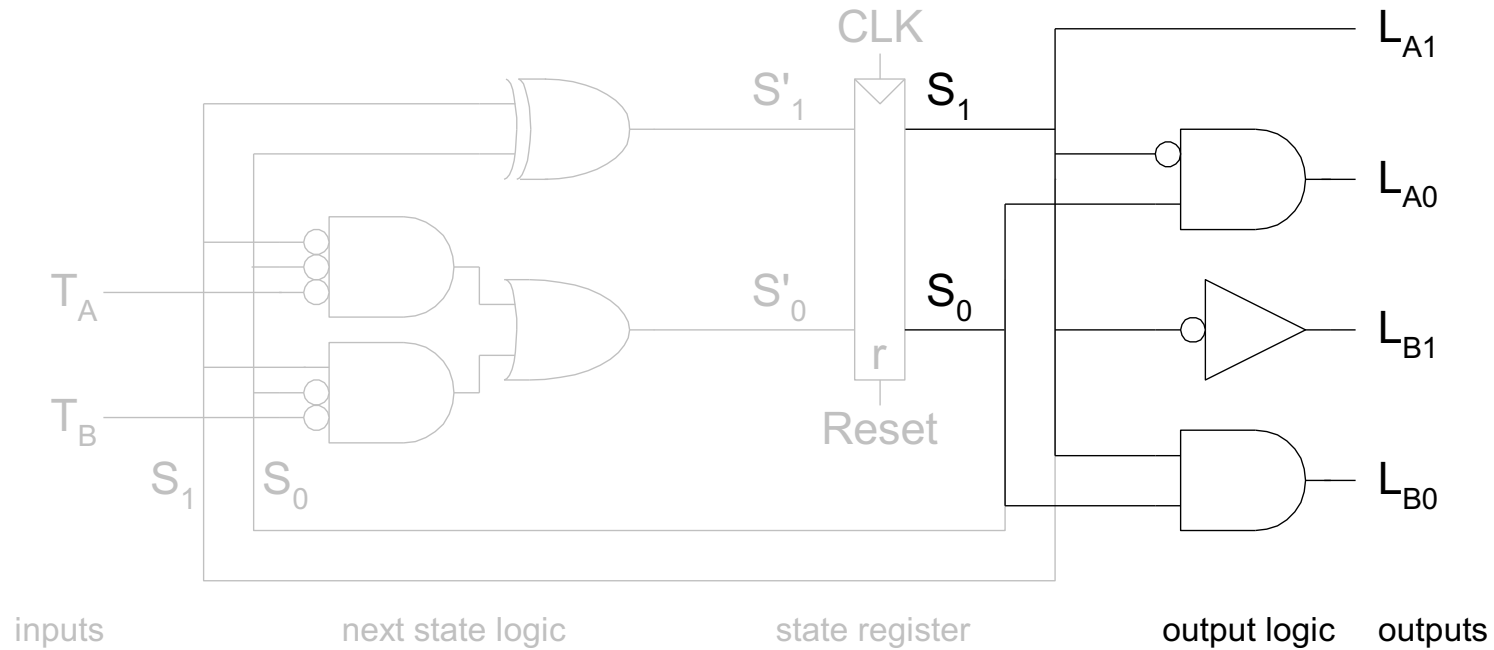


$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$



$$L_{B0} = S_1 \cdot S_0$$

# FSM Timing Diagram


 


CLK\_  
Reset\_  
T<sub>A</sub>\_  
T<sub>B</sub>\_  
S'<sub>1:0</sub>\_  
S<sub>1:0</sub>\_  
L<sub>A1:0</sub>\_  
L<sub>B1:0</sub>\_



# FSM Timing Diagram

  

# FSM Timing Diagram

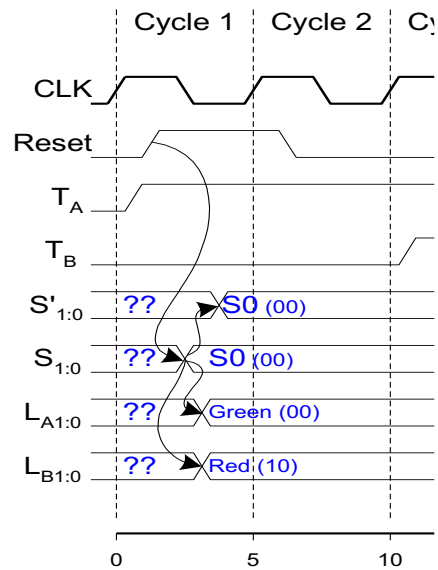
 


# FSM Timing Diagram

 
 






# FSM Timing Diagram

  


# FSM Timing Diagram

  


# FSM Timing Diagram

  



# FSM Timing Diagram

 

This is from H&H Section 3.4.1


 


# FSM Timing Diagram

  

# FSM Timing Diagram

See H&H Chapter 3.4

  


# Finite State Machine:

## State Encoding
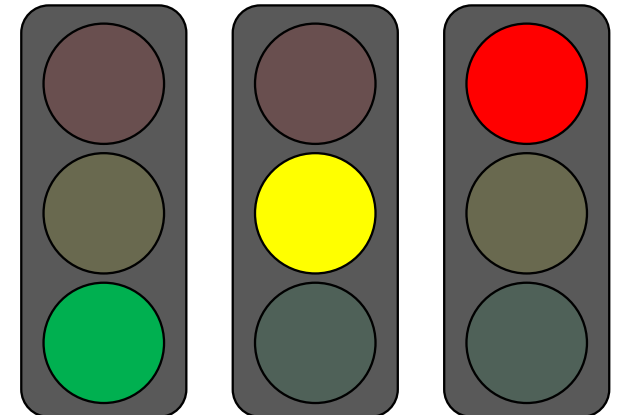
# FSM State Encoding

- How do we encode the state bits?
  - Three common state binary encodings with different tradeoffs
    - **Fully Encoded**
    - **1-Hot Encoded**
- Let's see an example traffic light with 3 states
  - Green, Yellow, Red





# FSM State Encoding

## 1. Binary Encoding (Full Encoding):

- Use the minimum possible number of bits
  - Use  $\log_2(\text{num\_states})$  bits to represent the states
- *Example state encodings:* 00, 01, 10
- **Minimizes** # flip-flops, but not necessarily output logic or next state logic

## 2. One-Hot Encoding:

- Each bit encodes a different state
  - Uses  $\text{num\_states}$  bits to represent the states
  - Exactly 1 bit is “**hot**” for a given state
- *Example state encodings:* 0001, 0010, 0100, 1000
- **Simplest design process** – very automatable
- **Maximizes** # flip-flops, **minimizes** next state logic

# FSM State Encoding

## 1. Binary Encoding (Full Encoding):

- Use the minimum possible number of bits

- Use

- *Example*

- **Minimizes**

## 2. One-Hot

- Each bit

- Use

- Exact

- *Example state encodings: 0001, 0010, 0100, 1000*

- **Simplest design process** – very automatable

- **Maximizes** # flip-flops, **minimizes** next state logic

The **designer** must **carefully** choose an encoding scheme to **optimize** the design under given constraints


logic

# Moore vs. Mealy Machines


# Recall: Moore vs. Mealy Machines

- Next state is determined by the current state and the inputs
- Two types of FSMs differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state
  - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 


Mealy FSM

 


Section 3.4.3 of H&H
 
# Moore vs. Mealy Examples

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.




Moore FSM

 


Example 3.7 of H&H
 
# Moore vs. Mealy Examples


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.



Moore FSM

 


Mealy FSM

 



# State Transition Diagrams

Moore FSM

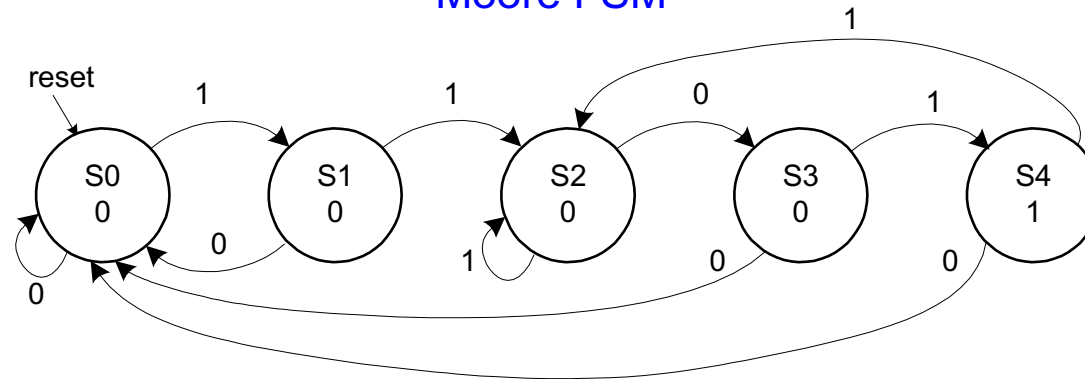

What are the tradeoffs?

Mealy FSM

  

# FSM Design Procedure (I)

## Step # 1: State transition diagram

- Formalize the specification and remove ambiguity

## Step # 2: Derive the next state logic

- Binary encoding for states
- State transition (truth) table
- Minimized Boolean equations for next state logic

## Step # 3: Derive the output logic

- Binary encoding for outputs
- Output table & Boolean equations

## Step # 4: Turn the Boolean equations into logic gate implementation

- Next state logic & output logic



# FSM Design Procedure (II)

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
  - Generally, this is done from a textual description
  - You need to:
    - 1) determine the **inputs** and **outputs** for each **state** and
    - 2) figure out how to get from one state to another
- **Approach**
  - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
  - Then continue to add **transitions** and **states**
  - Picking **good state names** is very important
  - Building an **FSM** is **like** programming (but it *is not* programming!)
    - An **FSM** has a sequential “control-flow” like a program with conditionals and goto’s
    - The if-then-else construct is controlled by one or more inputs
    - The outputs are controlled by the state or the inputs
  - In hardware, we typically have many concurrent **FSMs**

# Sync. Seq. Circuits: What We Covered Until Now


- The concept of state
- State diagrams
- Asynchronous vs. synchronous state changes
- Synchronous sequential circuits
- FSMs
  - Components, transition diagram, tables, equations, schematic
  - State transition diagrams
  - State encoding
  - Moore vs. Mealy
  - Design procedure

# Timing Issues in Sequential Circuits

Reading: Section 3.5 of H&H (More detailed than what we need in this course) 186

 
# Timing in Sequential Circuits

- We need to understand three aspects of timing specification
  - Clock-to-Q propagation delay
  - Setup time
  - Hold time


 
# Recall the Clock



- Output does not change instantly when the **rising edge** arrives
- Input needs to stay **stable** for some time for the flip-flop to take a **reliable** photograph



$$\text{Frequency} = 1/T_c$$

 
 
# Clock-to-Q Propagation Delay

- When the clock rises, the time it takes for the output to **settle** to the final value ( $t_{pcq}$ )



 
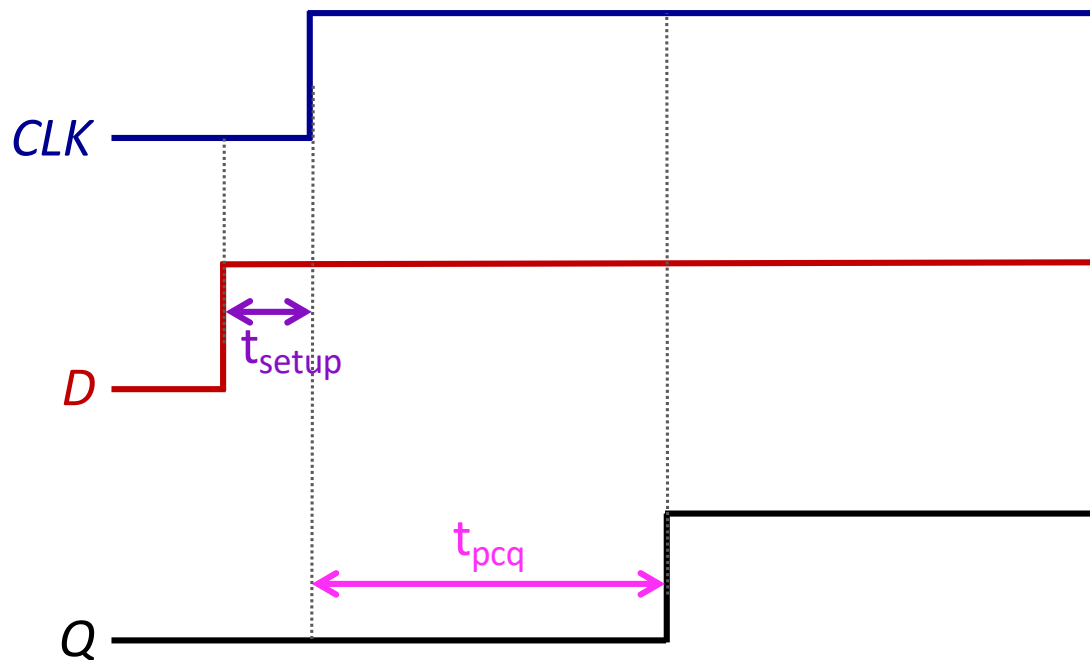
# Setup Time

- For the circuit to **sample** its input correctly, the input must have **stabilized** at least some setup time,  $t_{\text{setup}}$ , before the rising edge of the clock


 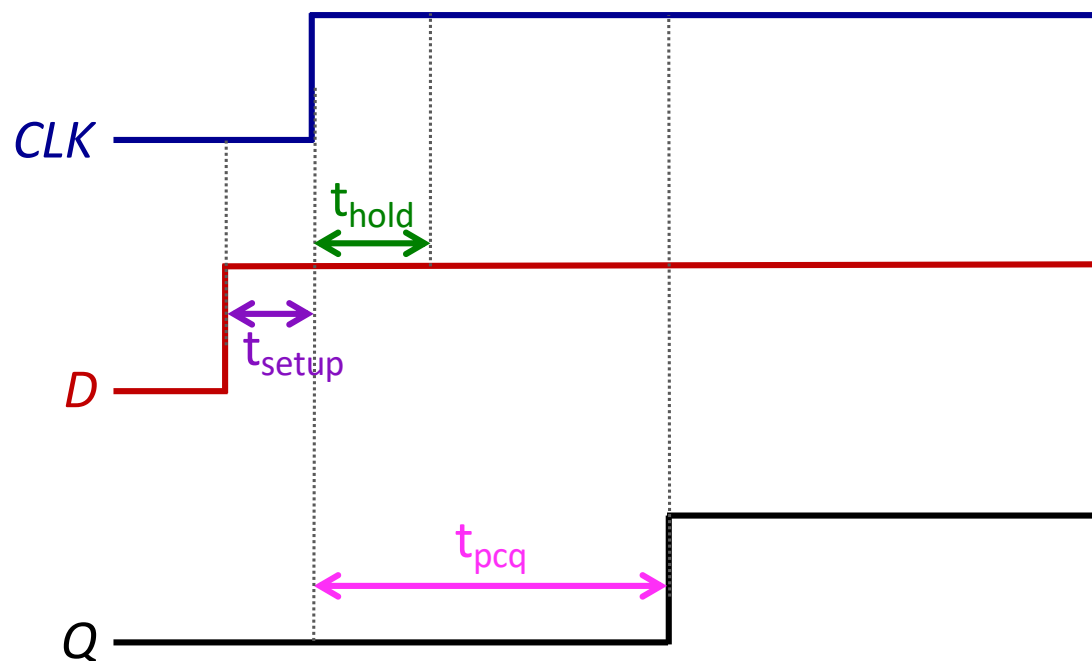
# Hold Time

- The input must remain **stable** for at least some hold time ( $t_{\text{hold}}$ ) after the rising edge of the clock





# Aperture Time

- The sum of the **setup** and **hold** times is called the aperture time of the circuit
- It is the **total time for which the input must remain stable**




# Technology and Hold Time

- It is a reasonable assumption that modern flip-flops have a **hold time** close to **zero**
- We can ignore hold time in subsequent discussions

# Example: Calculating Clock Period

- What is the **clock period** for the circuit below for it to work correctly in terms of  $t_{pd}$ ,  $t_{setup}$ , and  $t_{pcq}$  ?

$$T_c = t_{pcq} + t_{pd} + t_{setup}$$

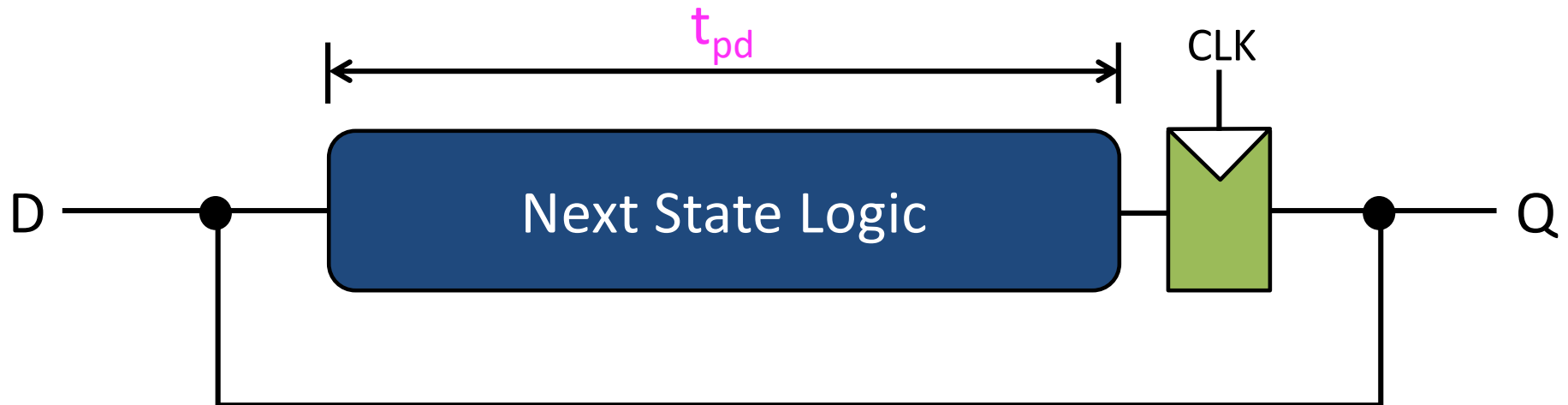


# Sequencing Overhead

- $t_{pcq} + t_{setup}$  is called the **sequencing** overhead of the flipflop
  
- $T_c = t_{pd} + t_{pcq} + t_{setup}$ 
  - Ideally, the entire **clock period** should be spent doing useful work (**processing done by the combinational circuit**)
  - The **sequencing** overhead of the flip-flop **cuts** into this time
 
# Recall: Synchronous Sequential Circuits

**General Rule:** *If the clock is sufficiently slow, so that the inputs to all registers settle before the next clock edge, all races are eliminated*



# Different Types of Storage Elements


# Diff. Storage Elements – Motivation

- **Flip-flops, registers, and flip-flop-based register files are used to make synchronous sequential circuits**
  - They process information based on current and past combinations of inputs
  - They have arithmetic circuits or logic elements to process inputs and history
  - Processing happens during a clock cycle, while state changes happen at the edge of clock (**synchronous**)
- **Sometimes, we just need to store lots of information**
  - Computer main memory, USB drives, Flash drives, etc
  - We can build cheaper storage elements that store information asynchronously – and processing happens somewhere else synchronously

 
# Example

Composed using ALUs, registers, muxes, and decoder to process one instruction every cycle

Just rows and rows of storage elements, and no cycle-by-cycle processing .... Just read and write words




CPU

 


Main Memory

 - On-chip fast memory called a L1/L2/L3 cache
- Subset of recently read data from main memory



Traditional Block Diagram of Computer

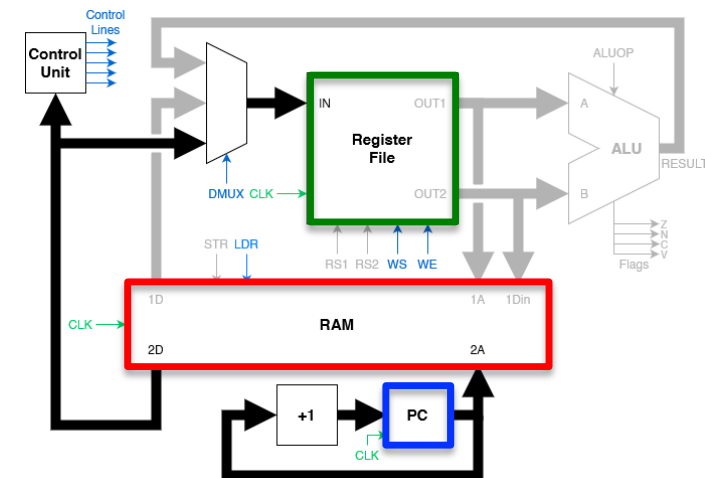




# Storage Elements

- **Latches and flip-flops**
  - **Very fast**
  - **Very expensive** (one bit costs tens of transistors)
- **Static RAM (SRAM)**
  - **Relatively fast**
  - **Expensive** (one bit costs **6** transistors)
- **Dynamic RAM (DRAM)**
  - **Slower than latches, flip-flops, and SRAM**
  - **Reading destroys content**, requiring a **refresh** operation to recharge the capacitor
  - **It needs a special process for manufacturing**
  - **Cheap** (one bit **costs only one transistor plus one transistor**)

Section 5.5 of H&H
 
# Generalized Storage Element


- Stores **one** bit (**bit cell**)
  - **Wordline enables** (**selects**) the storage element or bit cell
  - Bit line is used to **read** the stored bit or **write** a new bit



- Why is it called **word line**?
  - Word line **addresses** an entire (**unique**) word in a row of words
  - We **read** from and **write** to an entire row
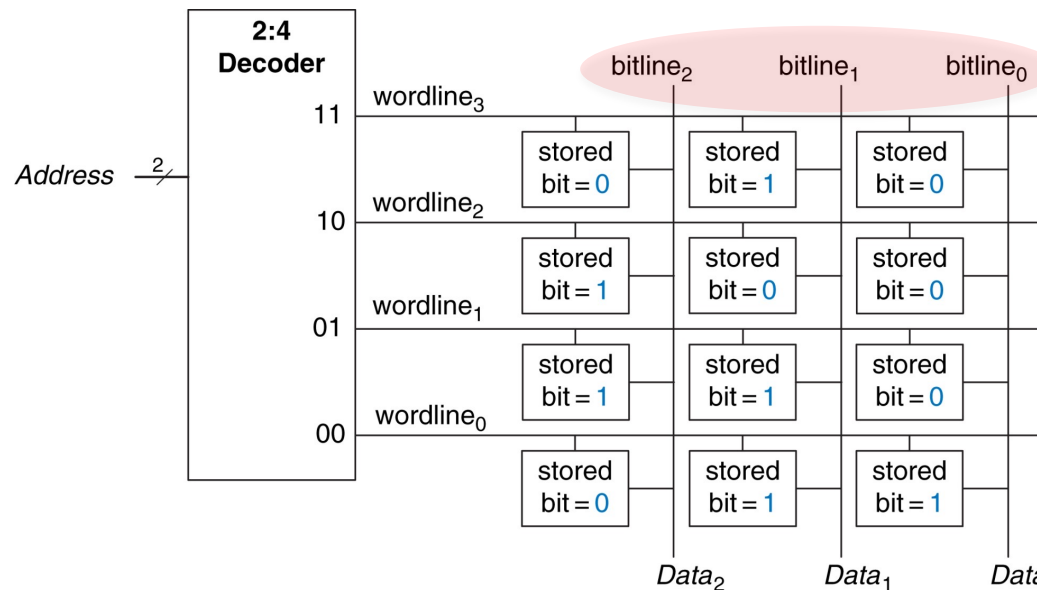
# Generalized Memory Organization

- A **decoder** to decode the output
- A **multiplexer** to select an output (**not shown below**)
  - Can also use **tri-state buffers** instead of AND/OR multiplexer




- Storage element can be of any "type"
- **Address/Data** makes up a **single port**

Section 5.5 of H&H

rightmost line  
is numbered 0
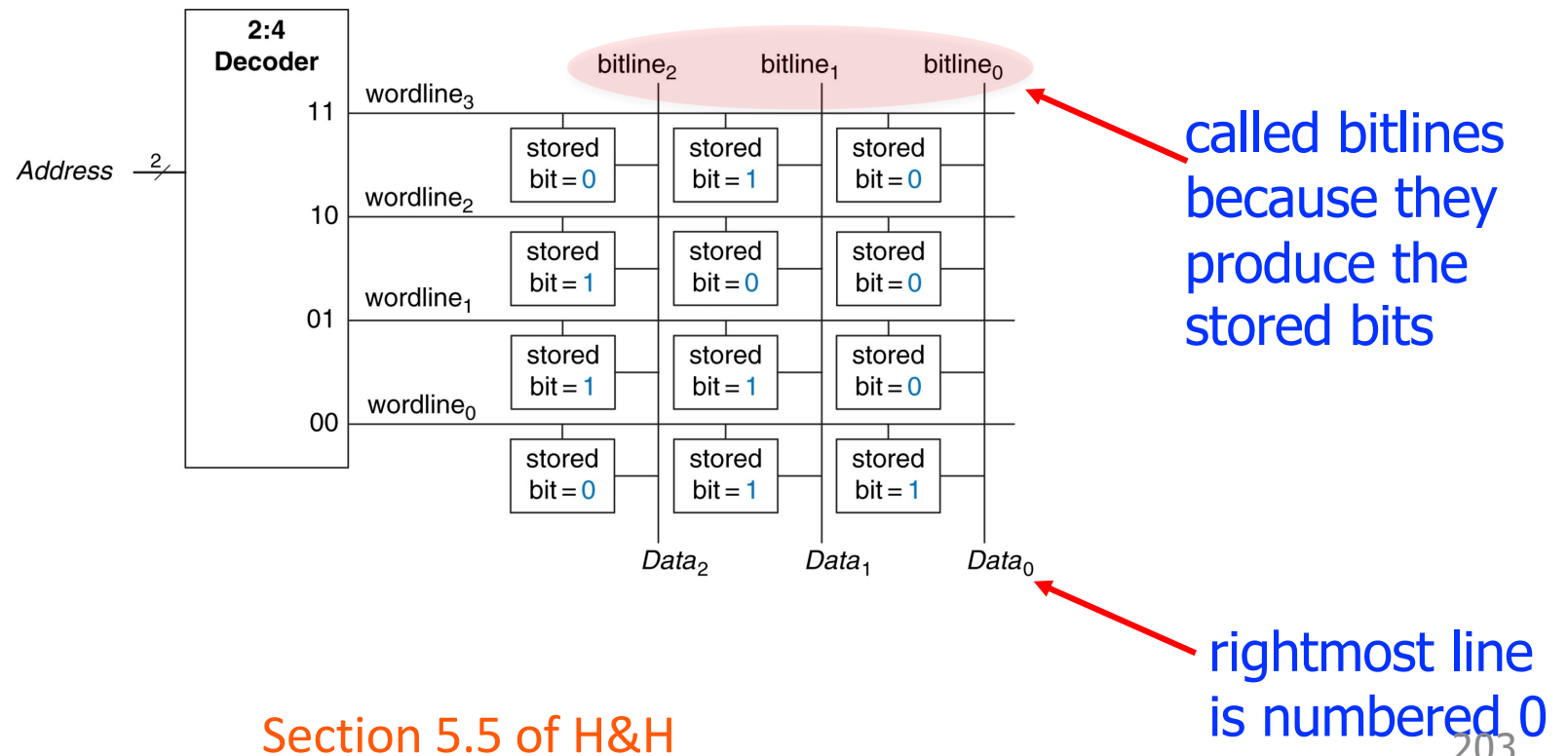
# Generalized Memory Organization

- Bitlines are used for both reading the stored bit and writing a new bit (circuit details of how it is done is outside scope)




# Read/Write Procedure in Detail

- **READ**
  - A **wordline** is asserted, and the corresponding row of bits cells drives the bitlines **HIGH** or **LOW**
- **WRITE**
  - The bitlines are driven **HIGH** or **LOW** first and then a **wordline** is **asserted**, allowing the **bitlines** values to be stored in that row of bit cells

# Recall a Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire

Tristate Buffer

 

$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1


**A tri-state buffer acts like a switch**

Figure 2.40 Tristate buffer

- **When E is LOW, output is a floating signal (Z)**
- **Floating:** Signal not driven by any circuit (open circuit, floating wire)


# Memory Port with Tri-State Buffer

Homework Exercise!

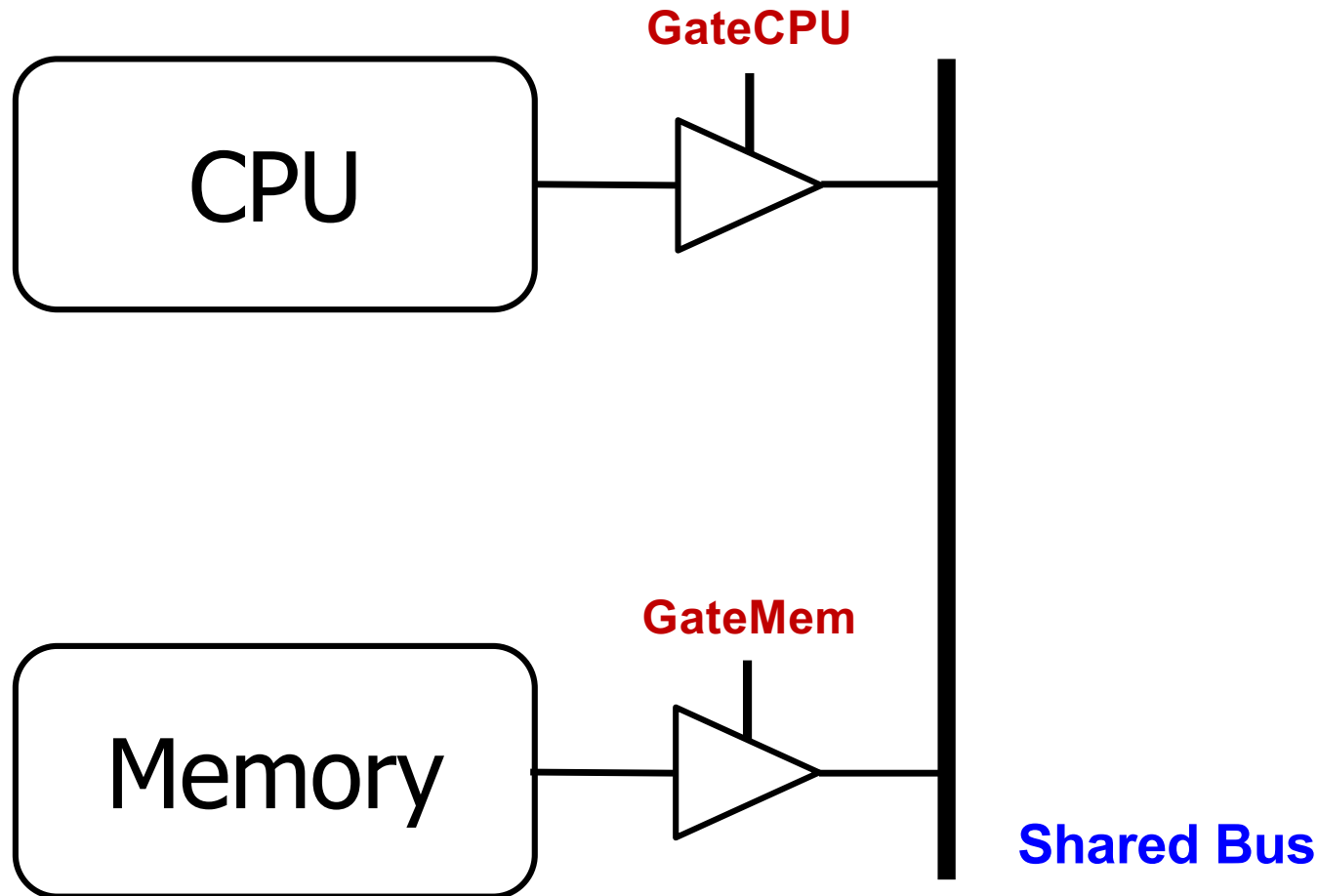
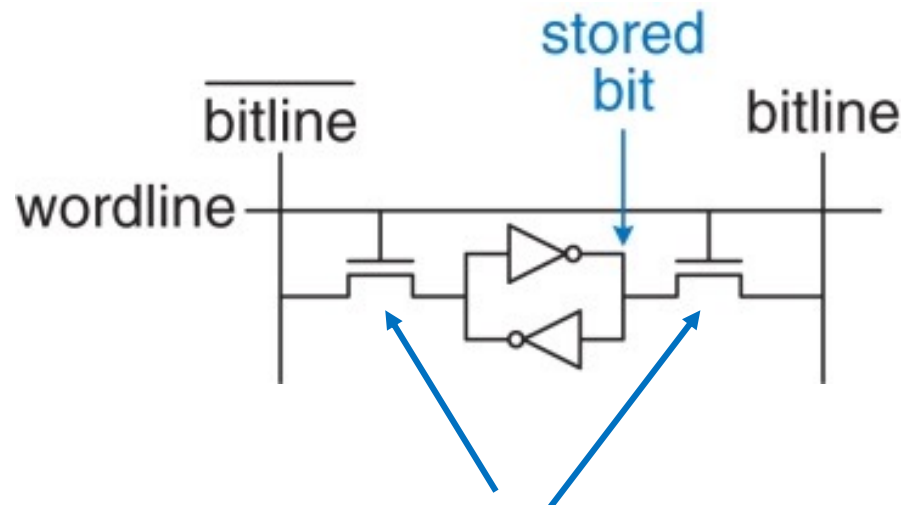
# SRAM Bit Cell


- **SRAM**: Static Random Access Memory
  - Data bit is stored in a cross-coupled inverter
  - Each cell has two outputs: bitline and **bitline** and **bitline**



- When the wordline is asserted, both nMOS transistors are turned **ON**, and data values are **transferred** to or from the **bitlines**




# SRAM Bit Cell

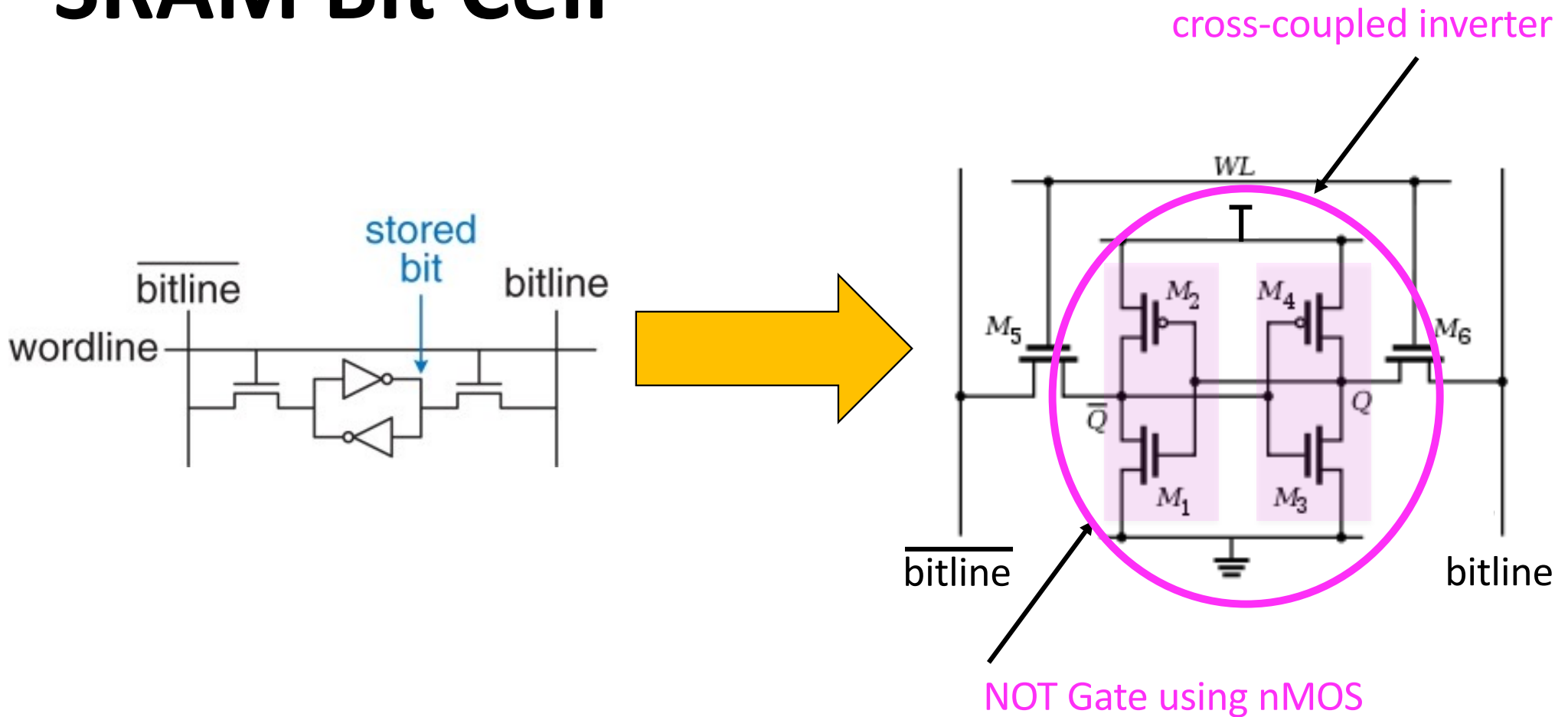

source: <https://electronics.stackexchange.com/questions/162466/how-do-the-access-transistors-in-an-sram-cell-work>
 
# Recall: MOS NOT Gate (Inverter)

- We have seen a NOT gate at the transistor level
  - If A = **0V** then Y = **3V**
  - If A = **3V** then Y = **0V**
- Interpretation of voltage levels
  - Interpret **0V** as logical (binary) **0** value
  - Interpret **3V** as logical (binary) **1** value



A	P	N	Y
0	<b>ON</b>	OFF	1
1	OFF	<b>ON</b>	0

$$Y = \bar{A}$$

# Random Access Memory (RAM)

- **RAM**: Random Access Memory
  - Each byte has an address (byte-addressable)
  - Any data word (*consisting of multiple bytes*) can be accessed independently of the other
  - **Any data word is accessed with the same delay as any other**

# Another Device for Storing Information

- What storage medium is this?



- A length of magnetic tape in a plastic enclosure with one or two reels for controlling the motion of the tape
- **Cassette used in tape recorders:** nearby data is accessed more quickly than faraway data
- **Inherently sequential device:** they must be rewound and read from the start to load data

# Yet Another Device for Storing Information

- What storage medium is this?






- A rotational platter with magnetic coating and arm assembly inside a casing
- **Hard disk used in all computers:** nearby data is accessed more quickly than faraway data
- **Inherently sequential device:** a disk must rotate under an arm for data to be read

# Random vs. Sequential access devices

These




vs.

These

  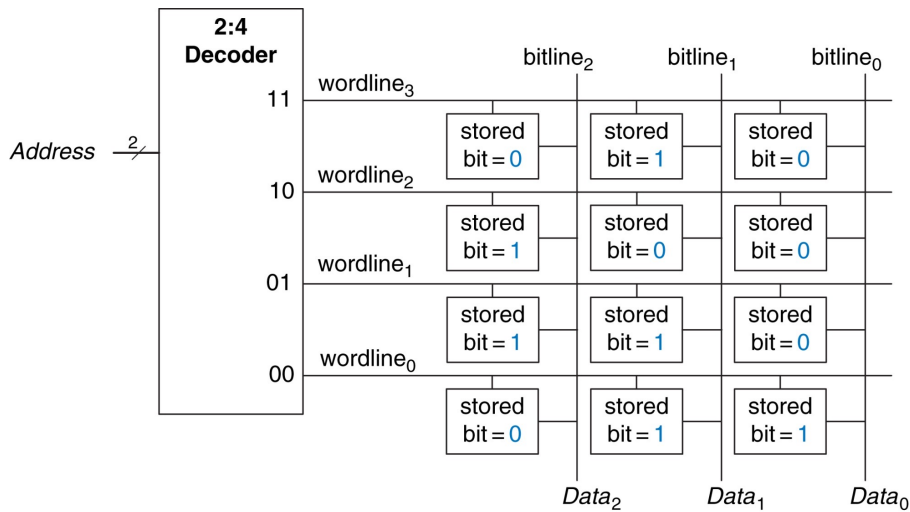
 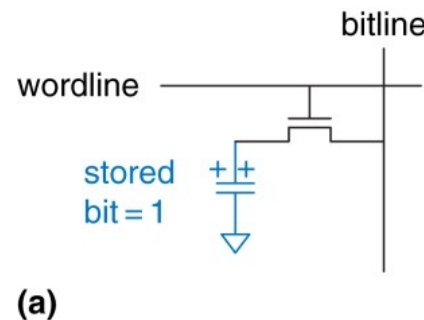 
# DRAM Bit Cell


- **DRAM**: **D**ynamic **R**andom **A**ccess **M**emory
  - Stores a **bit** as the presence or absence of a **charge** on a capacitor
  - The **nMOS** transistor behaves as a **switch** that either connects or disconnects the capacitor from the **bitline**




- When the wordline is **asserted**, the **nMOS transistor** turns **ON**, and the stored bit value **transfers to or from the bitline**
 
# Static vs. Dynamic

- Recall the **SRAM** cell: The **nMOS transistors** (M5 and M6) are driven by cross-coupled inverter connected to **supply voltage**
- **DRAM**: The capacitor node is not actively driven **HIGH** or **LOW** by a transistor tied to **supply voltage**



SRAM Cell

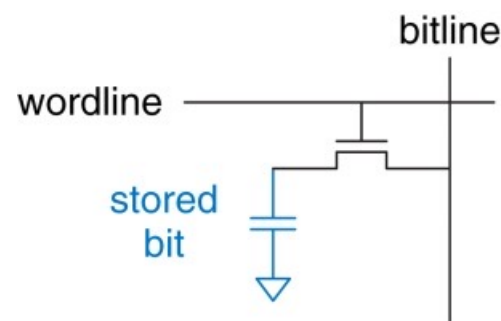


DRAM Cell


 
# DRAM Reads and Writes

- **Read:** Upon a **read**, data values are **transferred** from the capacitor to the bitline
  - **Reading destroys** the bit value stored on the capacitor, so the data word must be **restored (rewritten)** after each **read**
  - **Refresh:** Even when DRAM is not **read**, the contents must be **refreshed** (read and rewritten) every **few milliseconds**, because the charge on the capacitor gradually **leaks** away



- **Write:** Upon a **write**, data values are **transferred** from the bitline to the capacitor

# DRAM Refresh

- **Refresh:** Even when DRAM is not **read**, the contents must be **refreshed** (read and rewritten) every **few milliseconds** because *the charge on the capacitor* gradually **leaks** away
- **Refreshing consumes** extra energy
- **Refreshing** requires costly circuitry
  - It is a **critical drawback** of DRAM technology, especially at large capacities (many gigabytes, for example)


# Memory Comparison

- **Latches and flip-flops (20 transistors)**
  - **Very fast**
  - **Very expensive** (one bit costs tens of transistors)
- **Static RAM (SRAM) (6 transistors)**
  - **Relatively fast**
  - **Expensive** (one bit costs 6 transistors)
- **Dynamic RAM (DRAM) (1 transistor)**
  - **Slower than latches, flip-flops, and SRAM**
  - **Reading destroys content**, requiring a **refresh** operation to recharge the capacitor
  - **It needs a special process for manufacturing**
  - **Cheap** (one bit **costs only one transistor plus one transistor**)

Section 5.5 of H&H
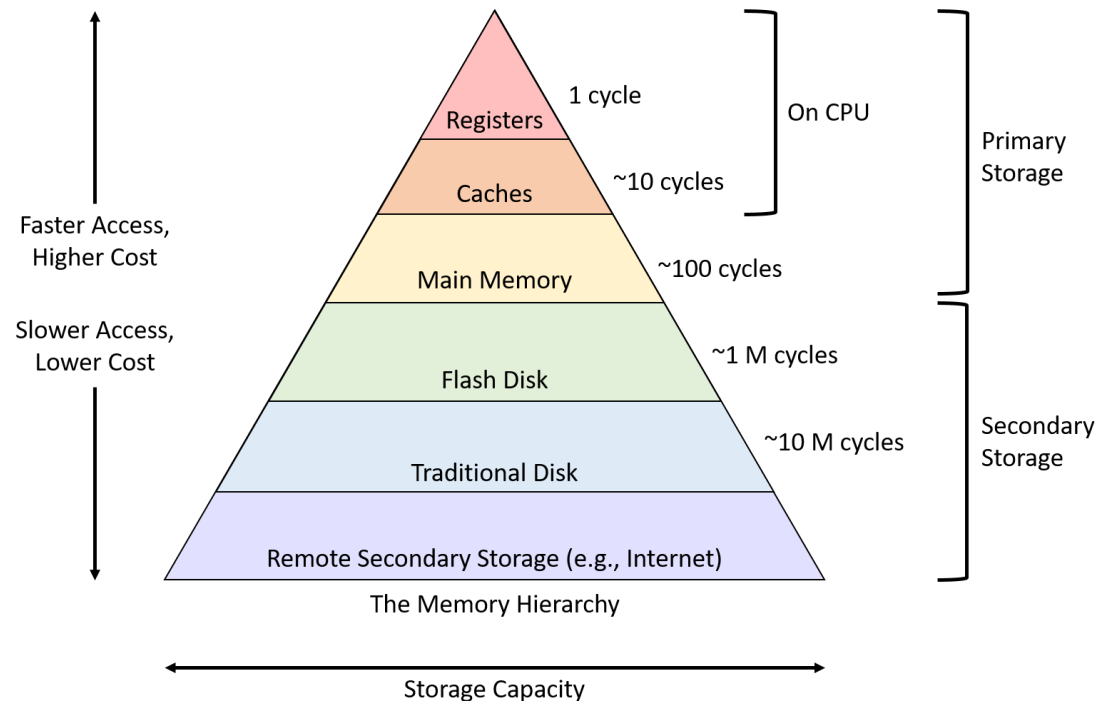
# Memory Hierarchy

- Large memories use **SRAM** and **DRAM**
- Registers inside the **CPU** use **flip-flops**



- Flip-flops are used in **synchronous sequential circuits (next)**